

**ME 210**

Team Pork Barrel

Brian Furciniti

Will Greenbaum

Rahul Sastry

Ying Zhao

# Project Planning

ME 210

0% 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 1 2 3 4 5 6 7 8 9 10 11 1

▼ Planning

- Brainstorming
- Acquiring parts
- Designing IR sensor circuits
- Designing movement circuit
- Design mechanical chassis
- Designing tape sensor circuits
- Strategy for defeating enemies
- Discuss software logic
- Design bumper (passive/active)

▼ Building


- PCB for IR sensors
- PCB for tape sensor
- Robot chassis
- Assemble motors and wheels
- PCB for motors to wheels
- Code up IR sensor in software
- Code up tape sensor logic
- Code up movement
- Test IR code
- Test tape sensing code
- Test movement code
- Test all individual parts

▼ Testing

- Test integration of all parts

▼ Perform!

- Beat the Brick
- Beat all enemies

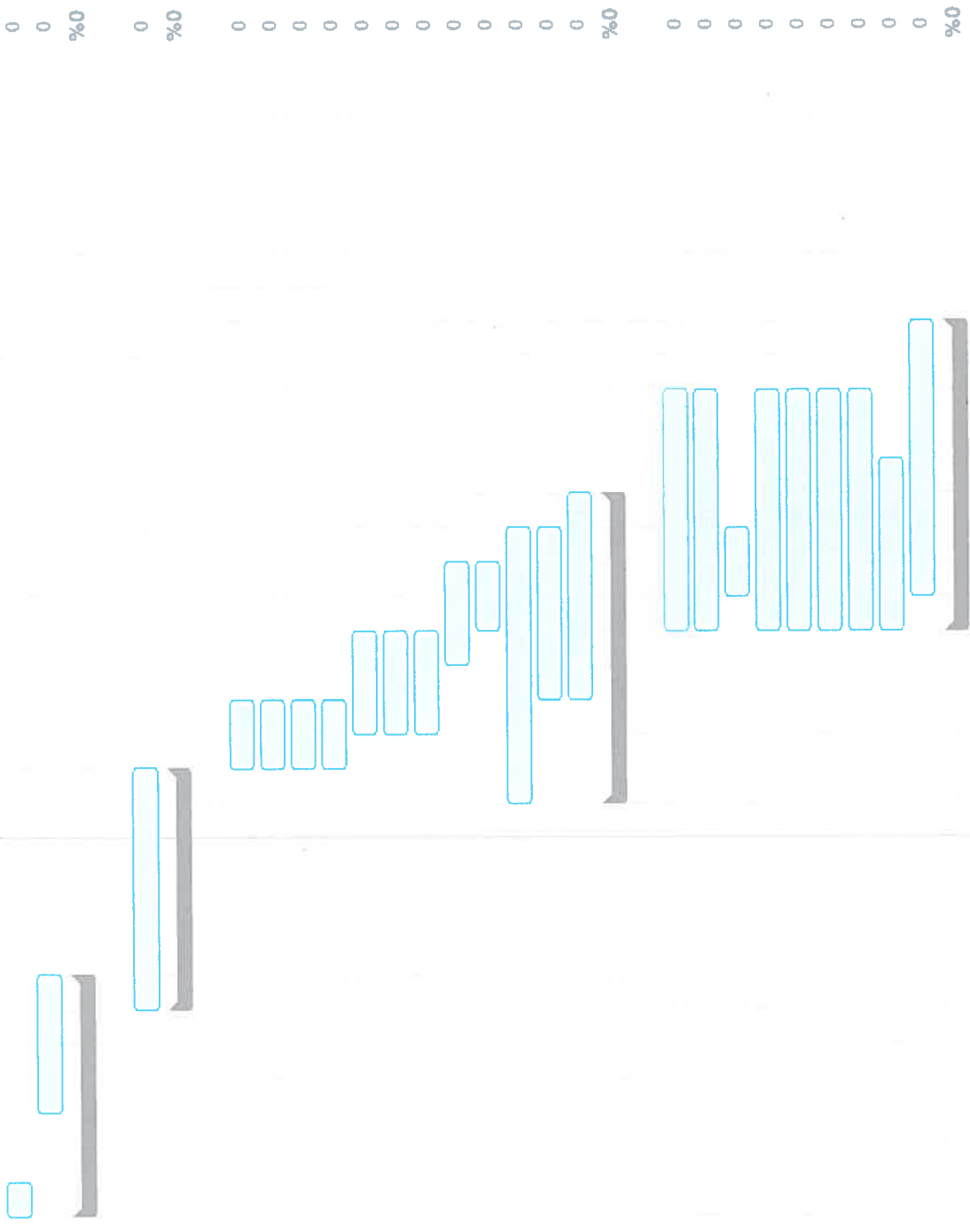


# Personnel Assignments



- Everyone:
  - Design IR circuit
  - Tape sensing design
  - Bumper design
  - Soldering and PCB
  - Strategy
- Rahul (shop access):
  - Source and spec motor
  - Sketch tape circuit
  - Coding up tape circuit
- Brian (shop access, car):
  - CAD up IR housing
  - Sketch the IR circuits
  - Code up IR sensing circuits
- Ying (Evil):
  - CAD/design robot chassis
  - Build the robot chassis out of Duron (1<sup>st</sup> prototype)
  - Code up movement logic
- Will (shop access):
  - Update HTML
  - Sketch bumper circuit (hall sensors?)
  - Physical bumper mechanism
  - Code bumper logic
- Nightly secret strategy meetings

IDEA # 1




# Bumpers

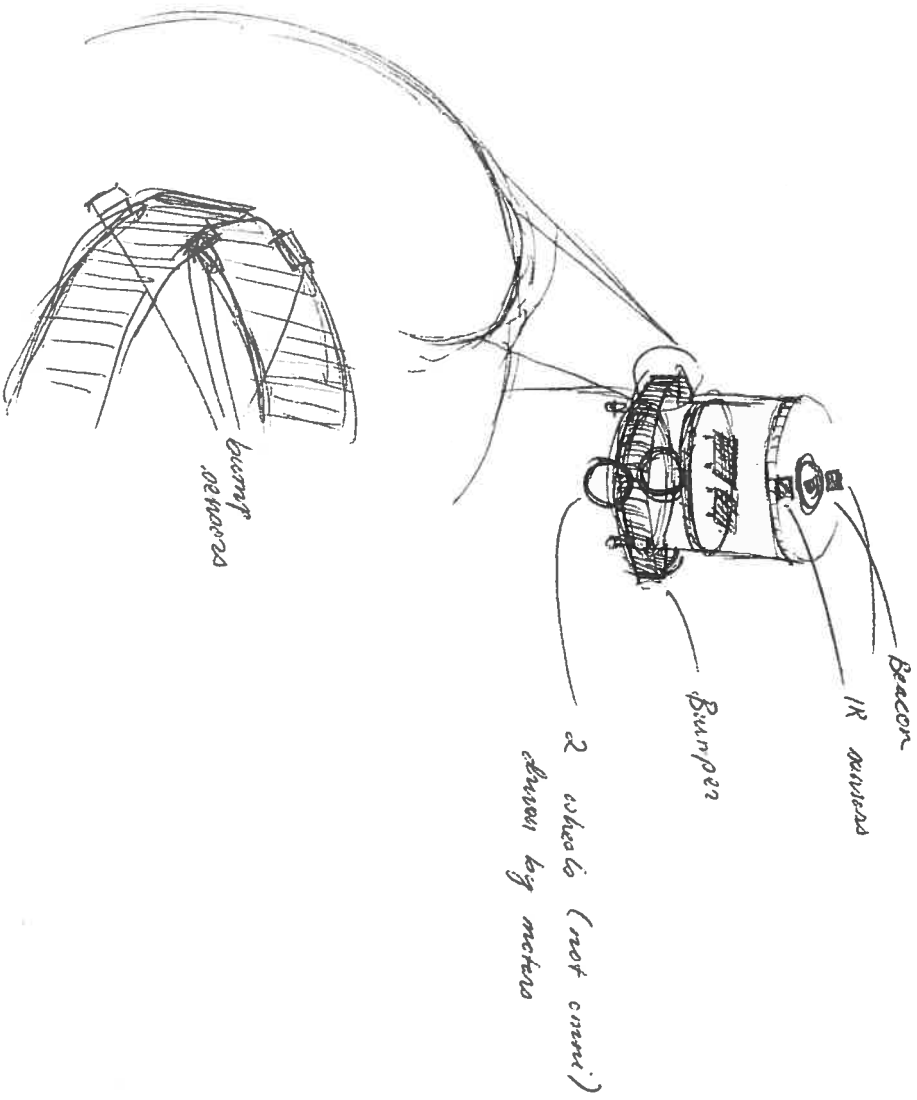

# Bumper Ideas

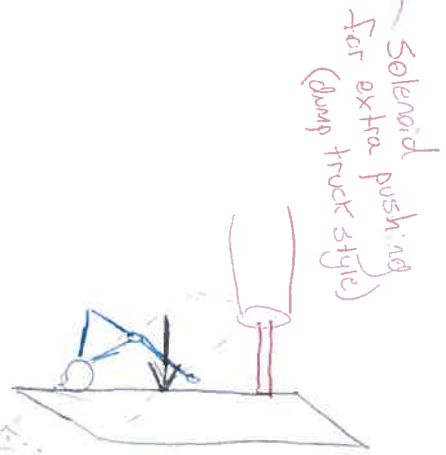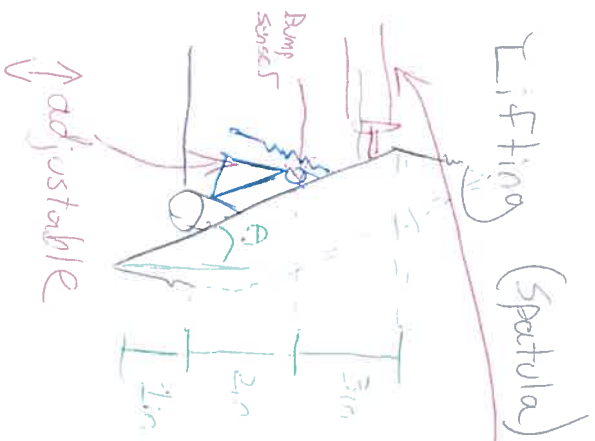

Cattle Guard

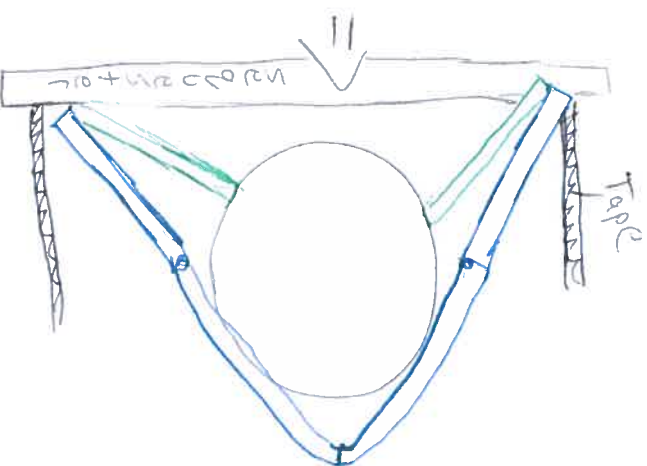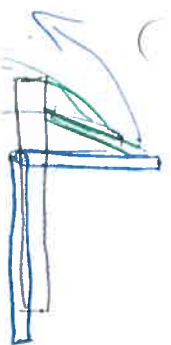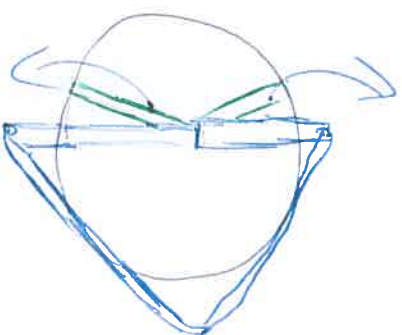


# IR Sensor

2/16/2015

Sensor | part

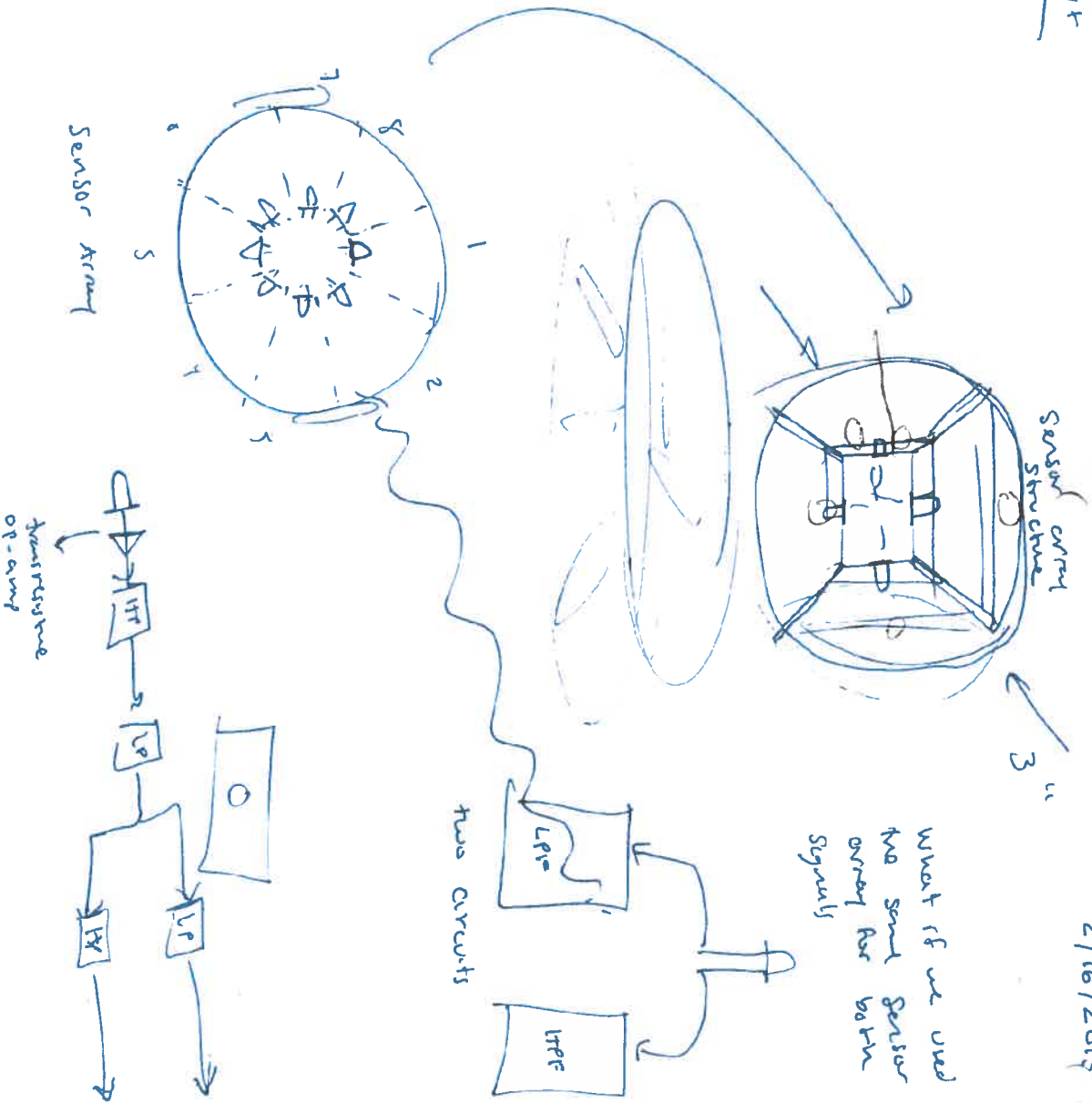
Servo  
Spinning  
 motor tracking  
 → radar




# Beacon and Sensor Housing

Sketch

2/11

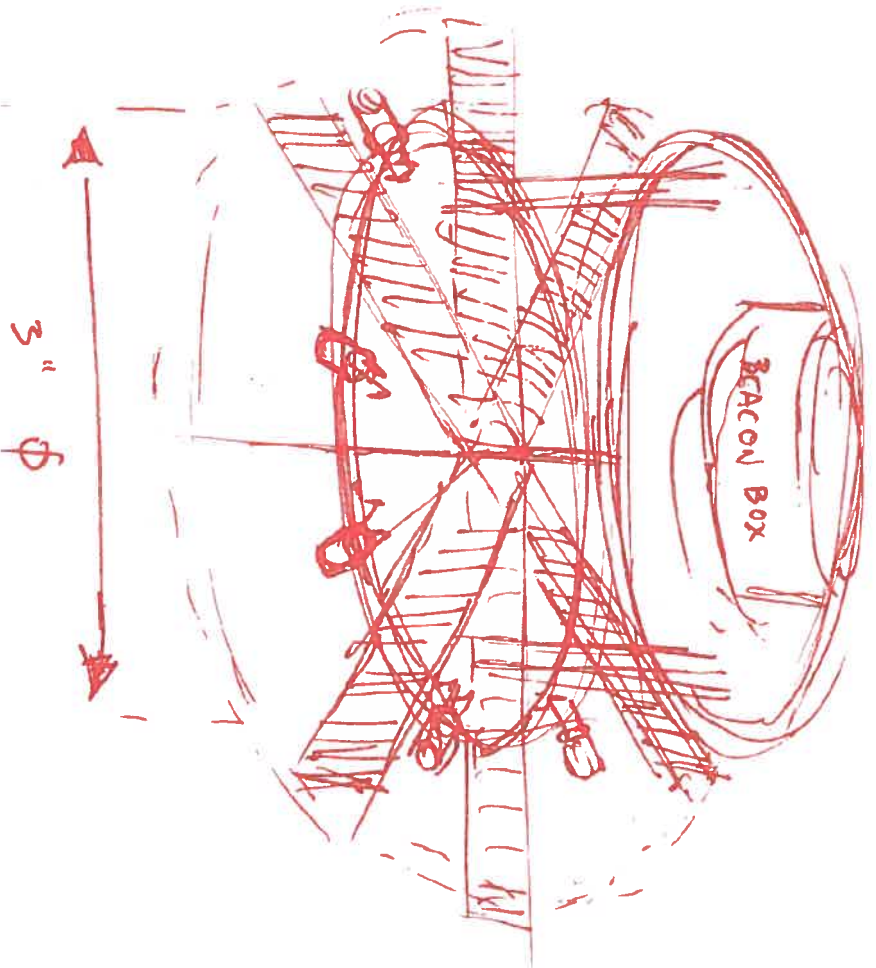


# Beacon Array Housing

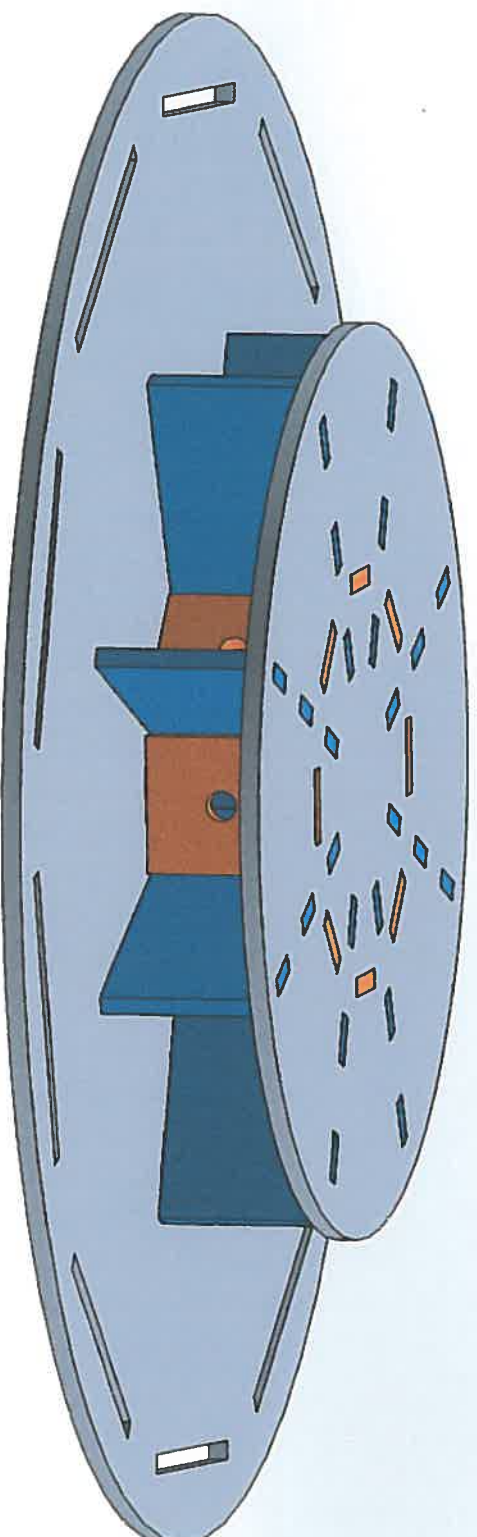




# Drive Systems

4 omni wheels

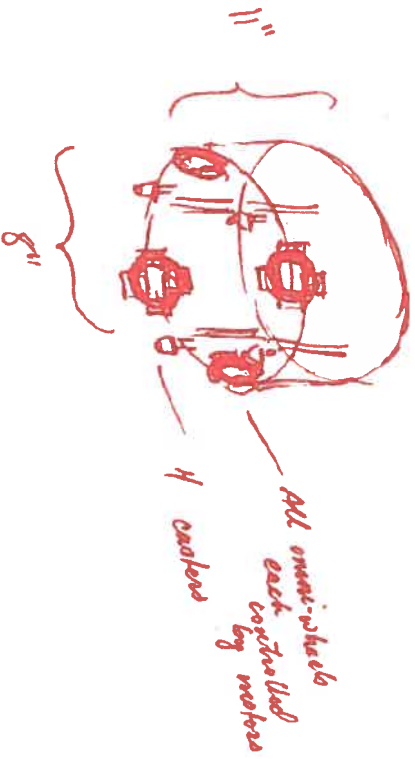

Treads

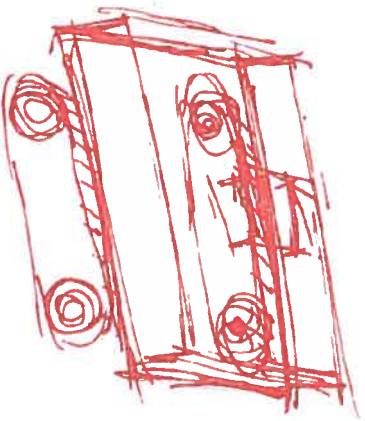


2 wheels



BASE ONLY

2/20/13

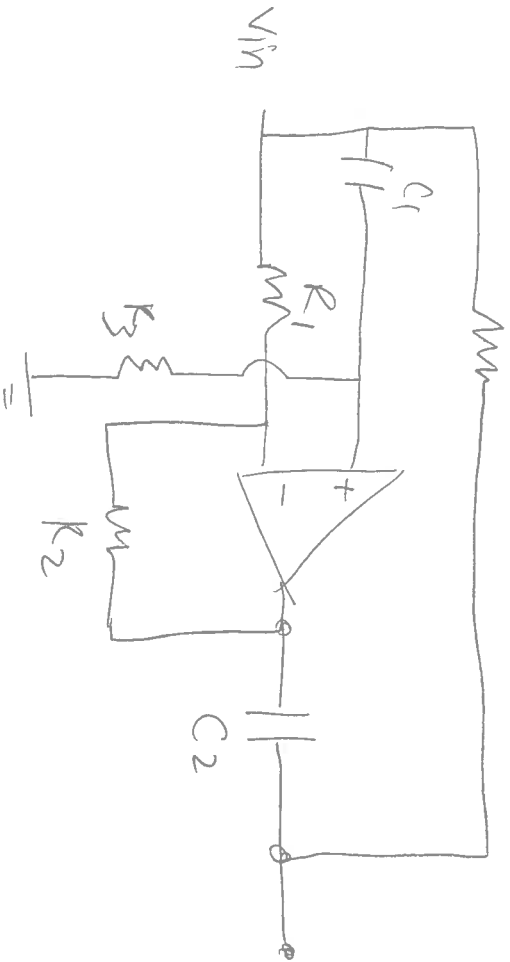

notch filter

850 Hz  
↙

$$f_{\text{notch}} = \frac{1}{2\pi RC}$$

$$R = R_3 = R_4$$

$$C = C_1 = C_2$$

$$R_1 = R_2$$

$$R_3 = R_4$$

$$C_1 = C_2$$

$$RC = \frac{1}{1900\pi} = .000187$$

$$C = 1\mu F$$


$$R_{3,4} = 187.241 \Omega$$

$$R_{1,2} = 10 k\Omega?$$

Callan-Ken

2/20/13

notch filter

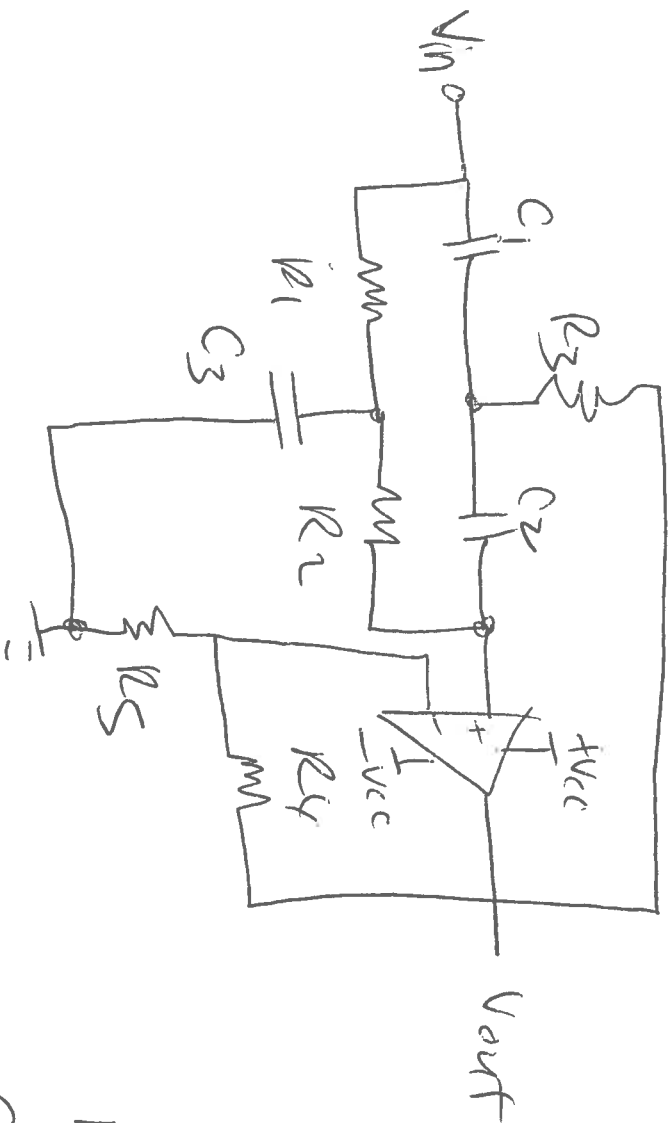

$$f = \frac{1}{2\pi RC}$$

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$R_3 = R/2$$


$$C_3 = 2C$$

$$R_4 \neq R_5$$

Standard  
values  
higher  
over 2



2 wheels

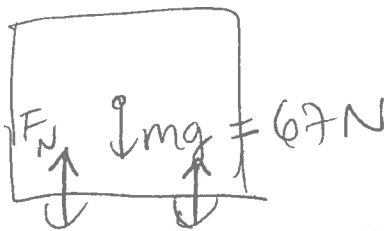

$$67 \text{ N} = 2F$$

3" diameter wheels

$$F_f = \mu N = .2 (67 \text{ N})$$

$$F_{fr} = .2 (N) = .2 (67)$$


$$r = .0381 \text{ m}$$

26.8 N force total


$$g = 9.81 \text{ m/s}^2 \quad \frac{1 \text{ kg}}{1000 \text{ g}} \quad \frac{9.81 \text{ m}}{\text{s}^2} \quad T = 1.021 \text{ Nm @ wheel}$$



$$\tau_{\text{motor}} = \tau_{\text{wheel}}$$
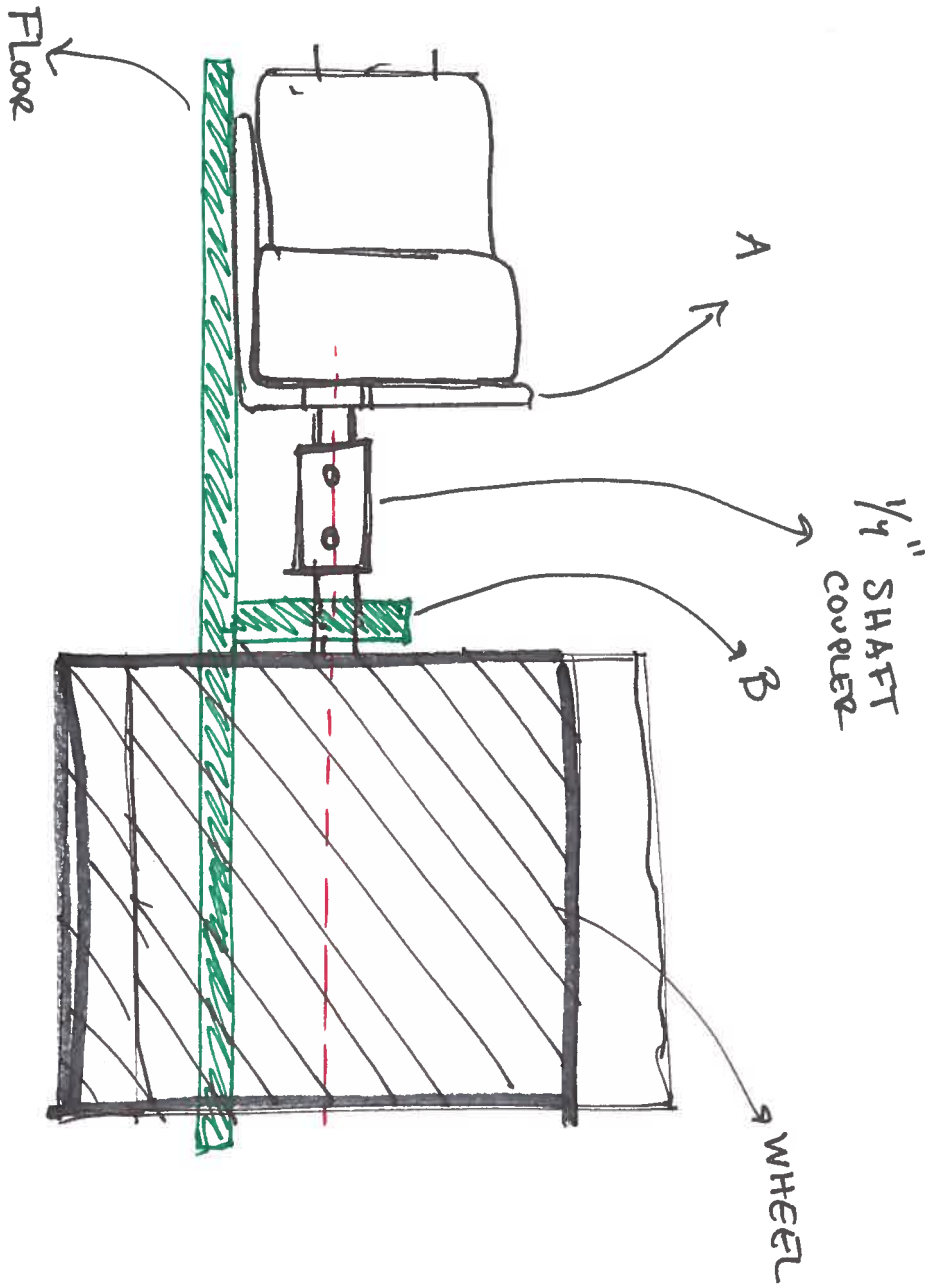
$$\frac{\tau_{\text{motor}}}{\tau_{\text{wheel}}} = \text{gear ratio} = \frac{\tau_{\text{wheel}}}{\tau_{\text{motor}}}$$




WHEEL INSERT

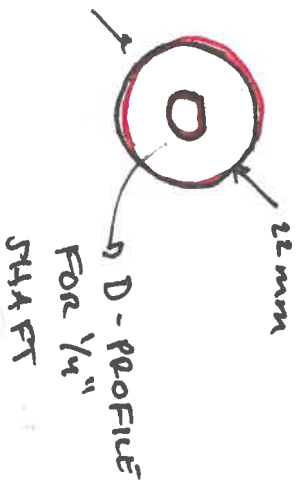


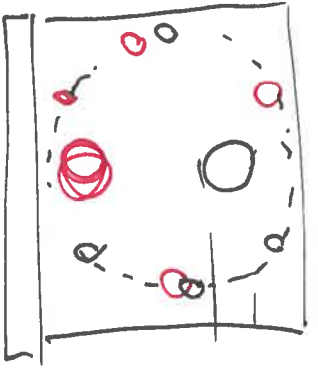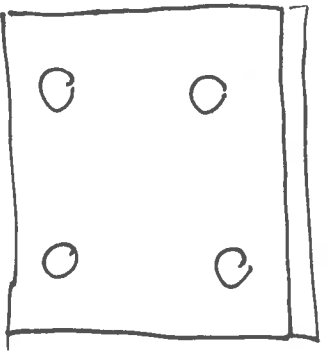

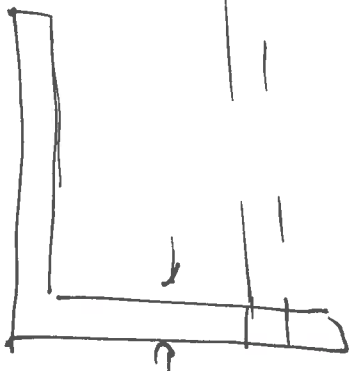A  
HOLES ACCORDING  
TO MOTOR  
DATA SHEET



$\frac{1}{8}$ " AL  
L-Stack

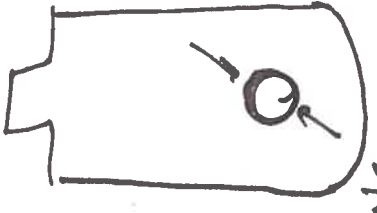



$\frac{3}{8}$ " hole  
for  
bearing

B






$\frac{5}{16}$ "  
Acrylic


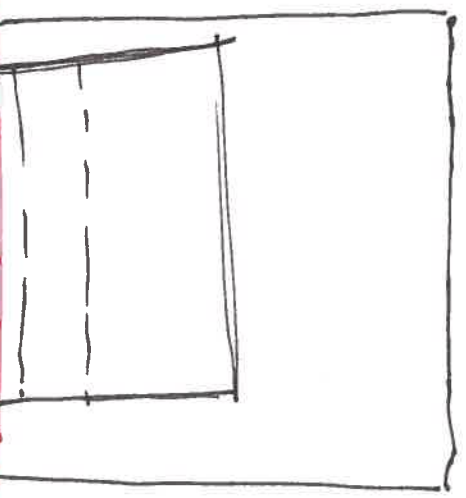


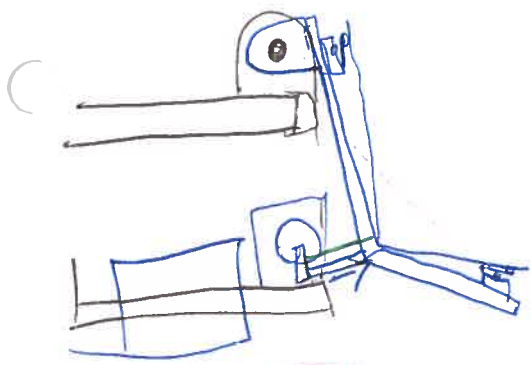

3 in

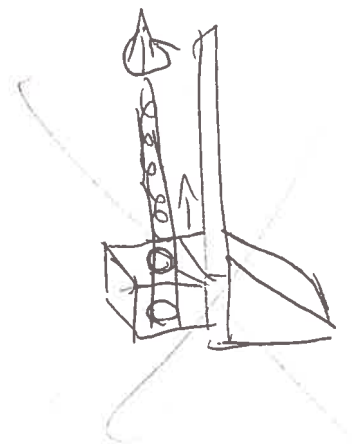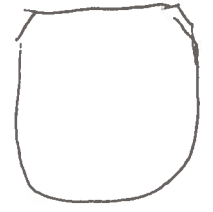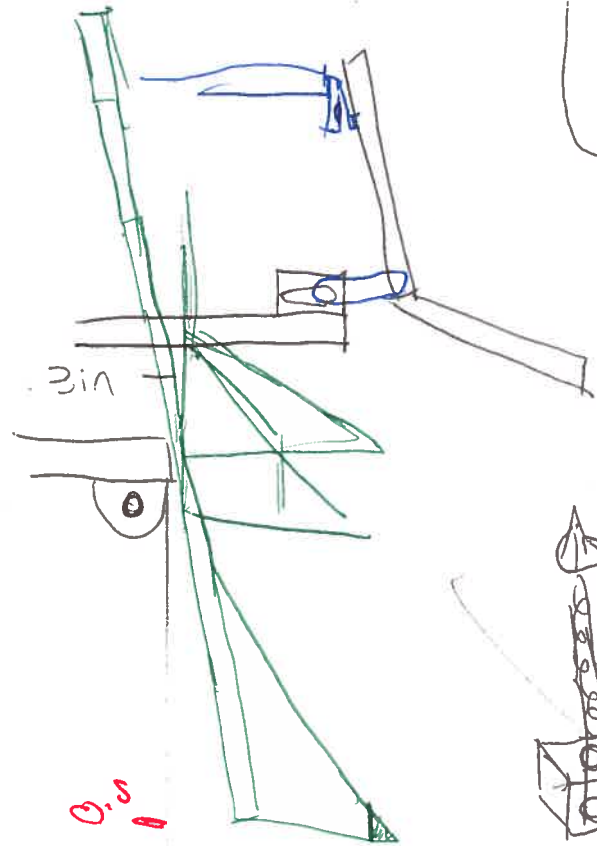

0.5  
floor ←

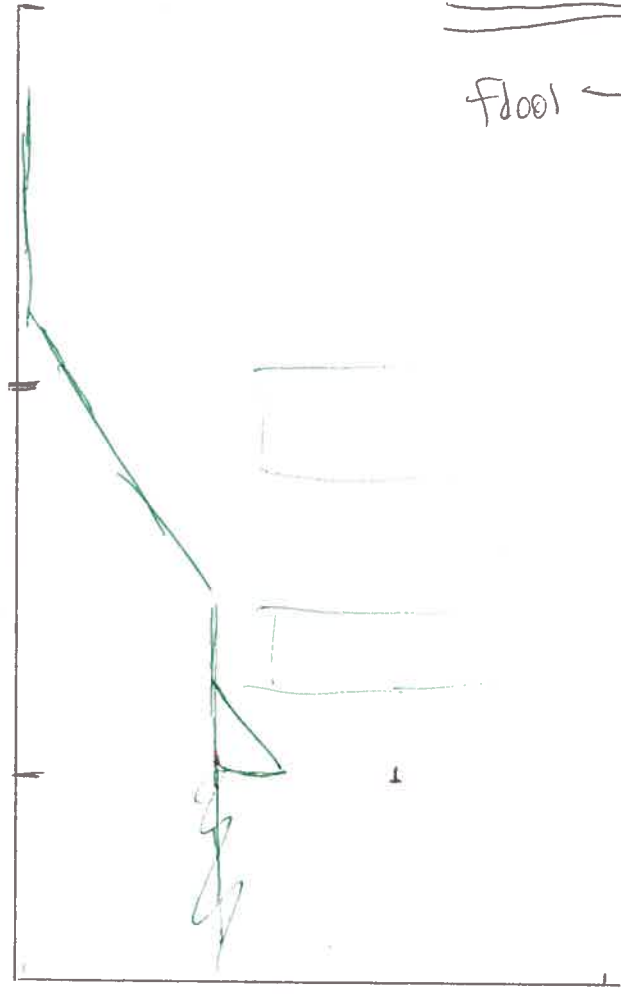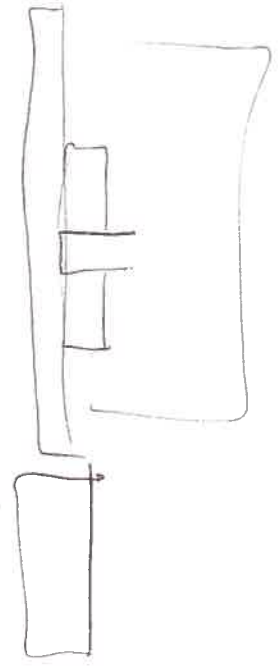

ground

# Reversible Gear Head Motors

JAMECO ReliaPro


## 6, 12 & 24VDC Reversible Gear Head Motors

\*Web Code: KBB

- Solder-type terminal
- High torque construction
- Dielectric strength: 300VDC
- Insulation resistance: 10MΩ
- Oil bearing design for long service life

### HN27GD Series


Part No.	Cross Ref. No.	Rated Voltage (VDC)	Operating Range (VDC)	@ Maximum Efficiency			Gear Ratio	Gear Case Size Dia. x Length (in.)	Motor Size Dia. x Depth (in.)	Shaft Size Dia. x Length (in.)	Pricing		
				Current (mA)	Speed (RPM)	Torque (g-cm)					1	5	25
167039	GH12-0953Y	12	4.5-24	90	9	1200	188:1	1.1 x 1.0	1.0 x 0.9	.16 x .60	\$18.95	\$16.95	\$15.25
249480	GH12-1213Y7-0	12	4.5-24	51	90	460	70:1	1.1 x 0.6	1.0 x 0.9	.16 x .60	19.95	18.95	17.95
167047	GH12-1828Y	12	4.5-24	195	31	1300	90:1	1.1 x 0.8	1.1 x 1.3	.16 x .60	23.95	21.95	19.95

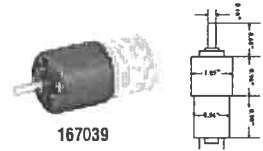

HN27GD Series

### GH30GM Series


Part No.	Cross Ref. No.	Rated Voltage (VDC)	Operating Range (VDC)	@ Maximum Efficiency			Gear Ratio	Gear Case Size Dia. x Length (in.)	Motor Size Dia. x Depth (in.)	Shaft Size Dia. x Length (in.)	Pricing		
				Current (mA)	Speed (RPM)	Torque (g-cm)					1	5	25
168438	GH12-1045Y	12	3.0-12	90	13	800	200:1	1.1 x 0.6	0.9 x 1.0	.16 x .70	\$15.95	\$14.95	\$13.95
170642	GH12-1828Y-10	12	6.0-24	105	8	3500	332:1	1.2 x 0.9	1.2 x 1.2	.16 x .70	22.95	19.95	17.95
150418	GH12-1921Y	12	4.5-12	200	25	2000	132:1	1.2 x 0.9	1.2 x 1.2	.16 x .70	23.95	21.95	19.95
162191	GH12-1324Y225	12	4.5-12	145	190	300	30:1	1.1 x 0.6	1.0 x 0.9	.16 x .70	17.95	15.95	13.95

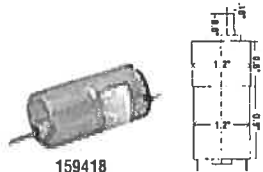

GH30GM Series

### 32GM Series


Part No.	Cross Ref. No.	Rated Voltage (VDC)	Current (mA)	Speed (RPM)	Torque (g-cm)	Gear Ratio	Gear Case Size Dia. x Height (in.)	Motor Size Dia. x Depth (in.)	Shaft Size Dia. x Length (in.)	Pricing		
										1	5	25
2146505	B32-6V3.1RPM	6	90	3	7350	340:1	1.9 x 0.41	1.3 x 0.9	.28 x .87	\$17.95	\$15.95	\$13.95
253323	B32-6V7RPM	6	40	6	1500	176:1	1.9 x 0.41	1.3 x 0.9	.30 x .70	12.95	11.49	9.95
323007	B2-902	6	38	8	1200	150:1	1.9 x 0.41	1.3 x 0.9	.30 x .70	17.95	15.95	13.95

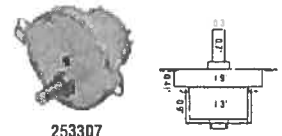

32GM Series

### 38GM Series

Part No.	Cross Ref. No.	Rated Voltage (VDC)	Current (mA)	Speed (RPM)	Torque (g-cm)	Gear Ratio	Gear Case Size Dia. x Length (in.)	Motor Size Dia. x Depth (in.)	Shaft Size Dia. x Length (in.)	Pricing		
										1	5	25
283534	38-010	12	97	24	7500	250:1	1.46 x 1.0	1.3 x 0.9	.24 x .50	\$16.95	\$14.95	\$13.49
253518	38-003	12	87.5	40	4800	150:1	1.46 x 1.0	1.3 x 0.9	.24 x .50	14.95	13.49	11.95
253500	38-007	12	82	60	3200	100:1	1.46 x 0.7	1.3 x 0.9	.24 x .50	17.95	15.95	13.95
253489	38-005	12	76	110	1300	56:1	1.46 x 0.7	1.3 x 0.9	.24 x .50	14.95	13.49	11.95
253471	38-004	12	74	120	1100	50:1	1.46 x 0.7	1.3 x 0.9	.24 x .50	14.95	13.45	11.95
253446	38-001	12	61.8	600	350	10:1	1.46 x 0.7	1.3 x 0.9	.24 x .50	17.95	15.95	14.49

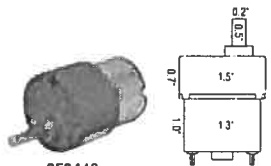

253446


38GM Series

### GH35GM Series Plastic Gears

Part No.	Cross Ref. No.	Rated Voltage (VDC)	Operating Range (VDC)	@ Maximum Efficiency			Gear Ratio	Gear Case Size Dia. x Length (in.)	Motor Size Dia. x Depth (in.)	Shaft Size Dia. x Length (in.)	Pricing		
				Current (mA)	Speed (RPM)	Torque (g-cm)					1	5	25
155012	GH12-1926Y	12	4.5-12	250	2	6000	3000:1	1.4 x 0.9	1.3 x 1.0	.23 x .90	\$24.95	\$22.49	\$19.95
155821	GH12-1830Y-P	12	4.5-12	220	4.5	4500	1000:1	1.4 x 0.9	1.3 x 1.0	.23 x .90	23.95	21.95	18.95
155839	GH12-1641T-L	12	3.0-12	250	20	3000	270:1	1.4 x 0.8	1.3 x 1.0	.23 x .90	25.95	22.95	19.95
152911	GH12-1926Y	12	4.5-12	172	40	2370	100:1	1.4 x 0.6	1.3 x 1.2	.24 x .90	24.95	22.49	19.95
155855	GH12-1641T-F	12	3.0-12	250	71	1000	60:1	1.4 x 0.6	1.3 x 1.0	.23 x .90	24.95	22.49	19.95
151441	GH12-1632TI	12	4.5-12	275	57	2200	100:1	1.4 x 0.6	1.3 x 1.0	.23 x .90	23.95	22.95	21.95
155863	GH12-1926Y-F	12	4.5-12	300	70	1000	60:1	1.4 x 0.7	1.3 x 1.0	.24 x .70	22.95	21.95	19.95
161374	GH12-1345T	12	4.5-12	185	116	850	30:1	1.3 x 0.9	1.5 x 0.7	.23 x .90	23.95	21.95	19.95
161382	GH12-1634T	12	4.5-12	293	145	850	30:1	1.4 x 0.6	1.3 x 1.0	.23 x .90	24.95	22.49	19.95
T64786	GH12-1640Y	12	4.5-24	120	220	180	10:1	1.4 x 0.6	1.3 x 1.1	.23 x .90	24.95	22.49	19.95
176050	GH12-1640Y00	24	12-24	340	1.8	6000	3000:1	1.4 x 1.0	1.3 x 1.0	.23 x .90	23.95	21.95	19.95
176032	GH24-1640Y06	24	12-24	340	50	2000	90:1	1.4 x 0.6	1.3 x 0.9	.23 x .90	25.95	22.95	19.95
176023	GH24-1640Y19	24	12-24	340	148	1000	30:1	1.4 x 0.6	1.3 x 0.9	.23 x .90	25.95	22.95	19.95



155012

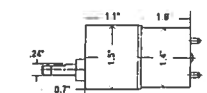

155013

GH35GM Series

### GH35GM Series Metal Gears

Part No.	Cross Ref. No.	Rated Voltage (VDC)	Operating Range (VDC)	@ Maximum Efficiency			Gear Ratio	Gear Case Size Dia. x Length (in.)	Motor Size Dia. x Depth (in.)	Shaft Size Dia. x Length (in.)	Pricing		
				Current (mA)	Speed (RPM)	Torque (g-cm)					1	5	25
155013	HN-GH12-1632T-R-M	12	4.5-12	250	2	6000	3000:1	1.3 x 0.9	1.5 x 1.1	.23 x .90	\$23.95	\$21.95	\$19.95
155822	GH12-1630Y-P-R-M	12	4.5-12	250	4.5	4500	1000:1	1.3 x 0.9	1.5 x 1.0	.23 x .90	23.95	21.95	18.95
151442	HN-GH12-1632T-R-M	12	4.5-12	275	57	2200	100:1	1.3 x 0.9	1.5 x 0.7	.23 x .90	22.95	20.49	17.95

### SOCCROBOTICS Gear Head Motor

- Current @ 6V: 57mA
- Stall current @ 6V: 633mA
- Stall torque @ 6V: 59.26 in. oz.
- Gear ratio: 143:1
- RPM @ 6V: 80
- Size: 2.2"L x 1.9"W x 0.9"H



Part No.	Mfr. Part No.	1	5	25
400995	GMB	\$6.95	\$6.25	\$5.75

### Gear Head Motor Pair w/ 90° Shaft

- Recommended voltage: 4.5VDC
- No load speed: 90 RPM ±10
- No load current: 190mA (max. 250mA)
- Torque: 800 gf cm (min.)
- Size: 2.5"L x 1.5"W x 0.9"H



Part No.	Mfr. Part No.	1	5	25
2150432	DG01D	\$6.49	\$5.95	\$5.49

### Pololu Miniature Gear Motor

- Input voltage: 6V
- Gear ratio: 100:1
- Free-run speed @ 6V: 320 RPM
- Stall torque @ 6V: 25 oz-in.
- Size: 0.94"L x 0.39"W x 0.47"H
- Weight: 0.34 oz.



Part No.	Mfr. Part No.	1	5
2128219	1101	\$15.95	\$14.95


\*For additional products, availability, and additional specifications visit [Jameco.com](http://Jameco.com) and enter the web code in the product search box

NAME BRANDS	4 LEVELS OF SAVINGS	HOUSE BRANDS	FACTORY OVERRRUN	DOLLAR SALE
-------------	---------------------	--------------	------------------	-------------


Order by Phone at 1-800-831-4242 or Online at [www.Jameco.com](http://www.Jameco.com)



# VOLTAGE REGULATOR

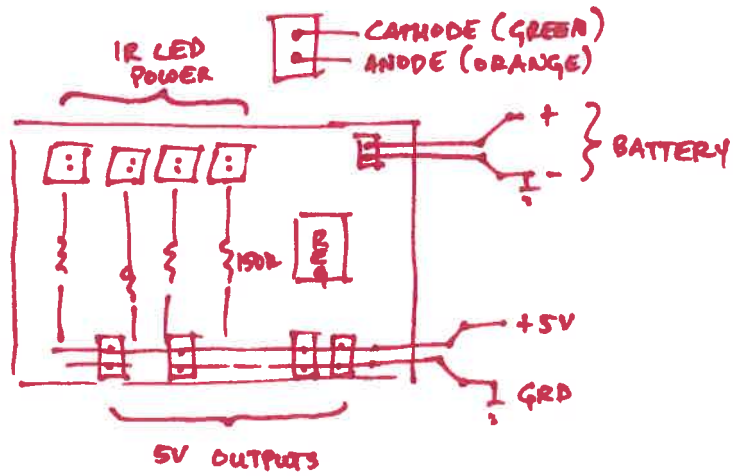


REG:

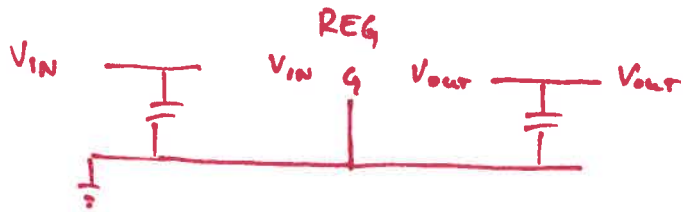

SOURCES  $\leq 1 A$

LED:

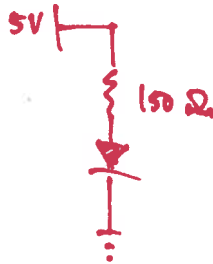

$$I_{NL} = 65 \text{ mA}$$

$$\tau_R = 3.2 \text{ kg}\cdot\text{cm} = 3200 \text{ N}\cdot\text{m}$$

$$\omega_R = 60 \text{ RPM}$$

$$I_{IL} = 82 \text{ mA}$$

$$\omega_{NL} = 72$$

$$\omega = \frac{\tau_2}{\tau_1} - \frac{12/3200}{\tau_2} \tau$$

$$(0.07) \left( \frac{11.3 \text{ kg}}{25 \text{ lb}} \right) (9.8 \text{ m/s}^2) = 7.77 \text{ N}$$

$$R = 0.035 \text{ m}$$

$$0.2723 \text{ N}\cdot\text{m}$$

$$= 2723 \text{ gcm}$$

$$-0.3182 \quad +91.091$$

$$\omega = \sqrt{48 - \frac{4800}{40}}$$

$$\tau = kI \text{ Hz}$$

$$I = I_{static} - C \omega_{rem}$$



$$I = 65 \text{ mA} - k\omega$$

$$\omega = 60 \quad I = 82$$


$$\omega = 72 \quad I = 65$$

# Motor Drivers

LMP18200 3A

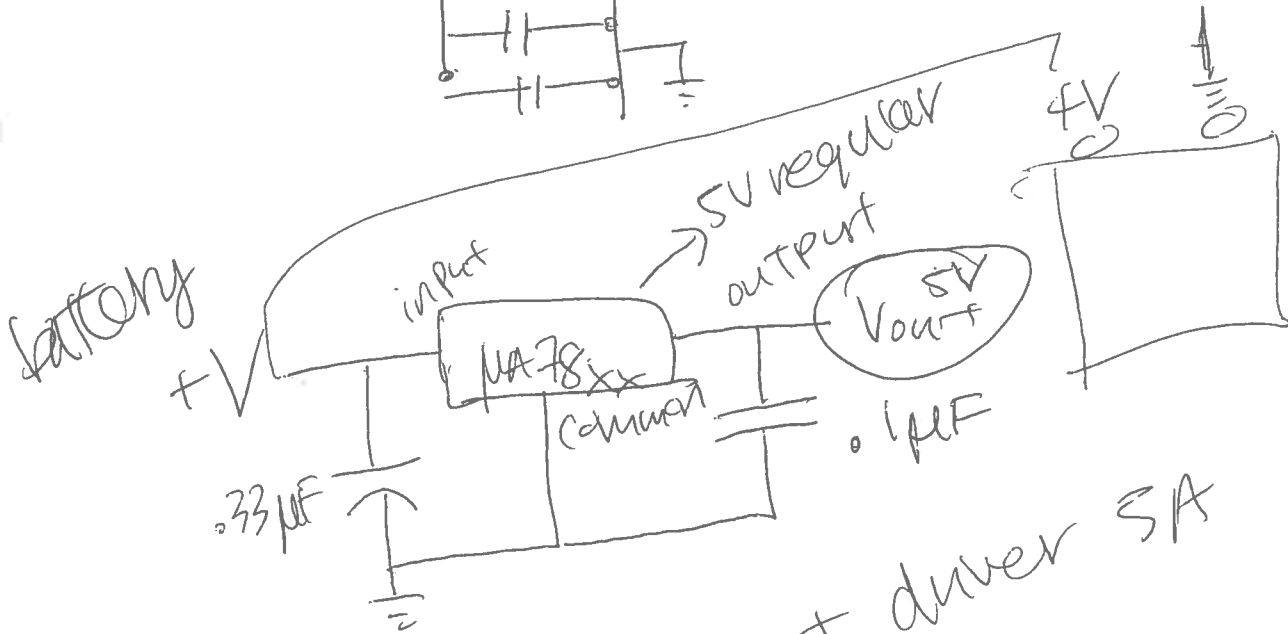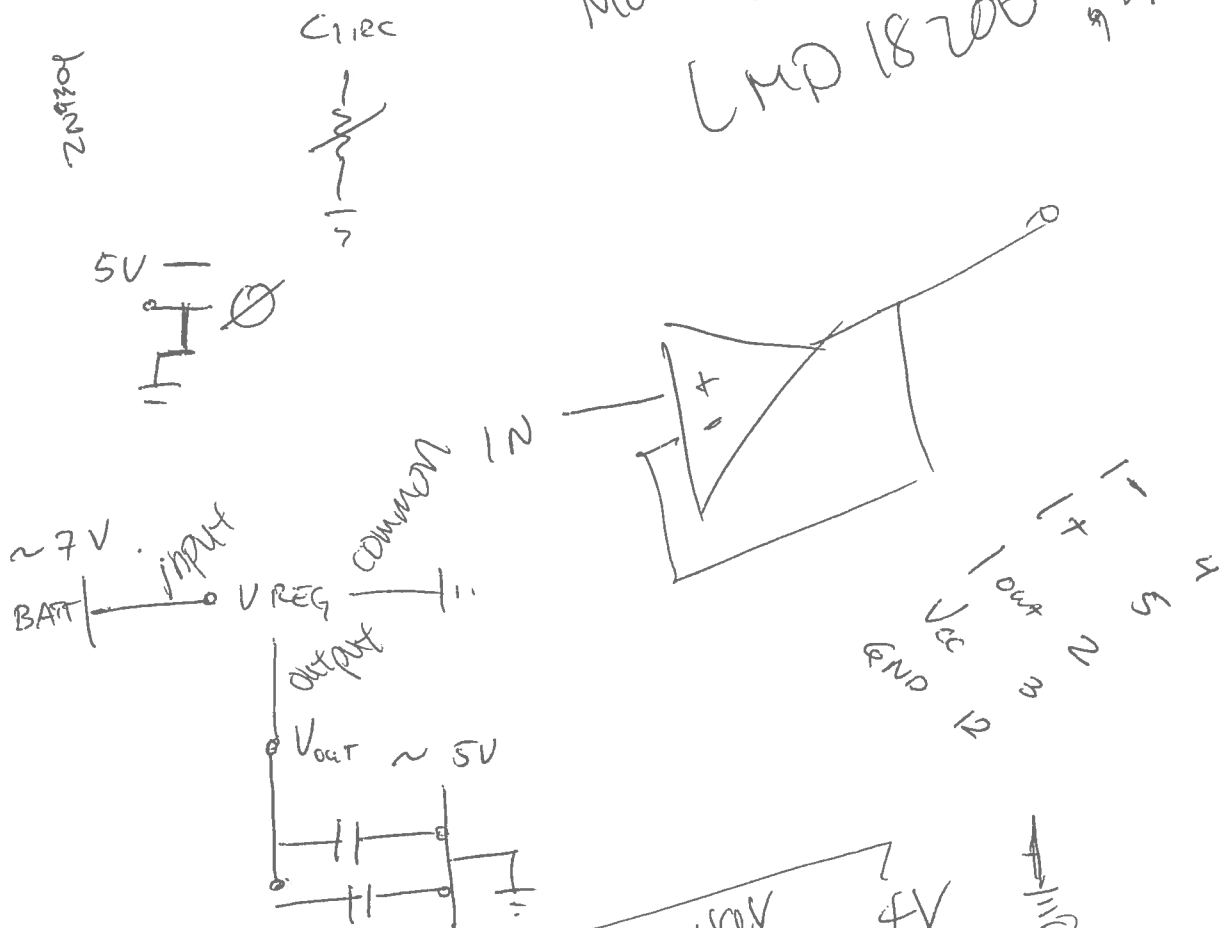

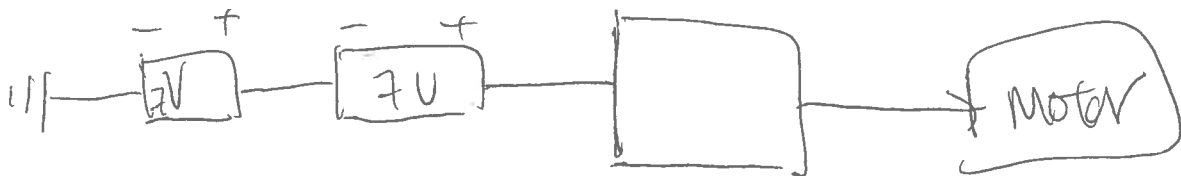
current driver SA  
 HV driver → NCV7729 - 8A




# H-BRIDGE BOARD
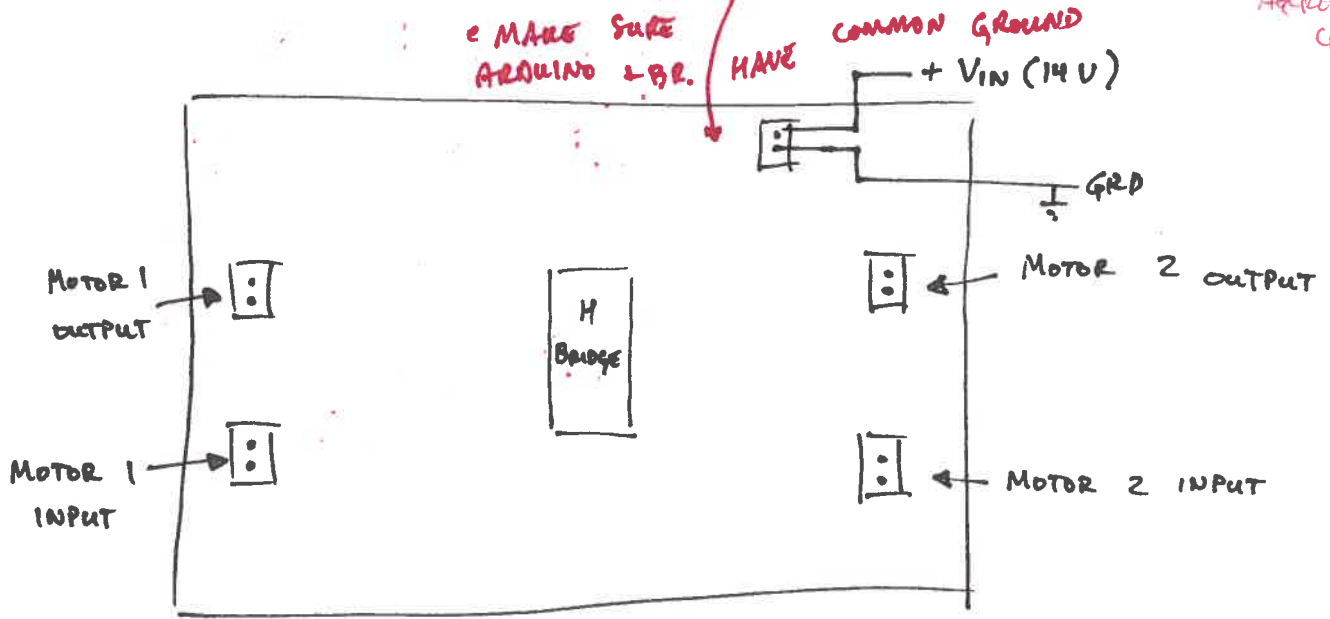
## To do

- ADD A BIG <sup>CAPACITOR</sup> ~~BRIDGE~~ HERE (ACROSS RAILS) + SMALL ONE ACROSS CHIP
- THERMAL GREASE
- MAKE SURE ARDUINO +5V. HAVE COMMON GROUND




# TAPE SENSING BOARD

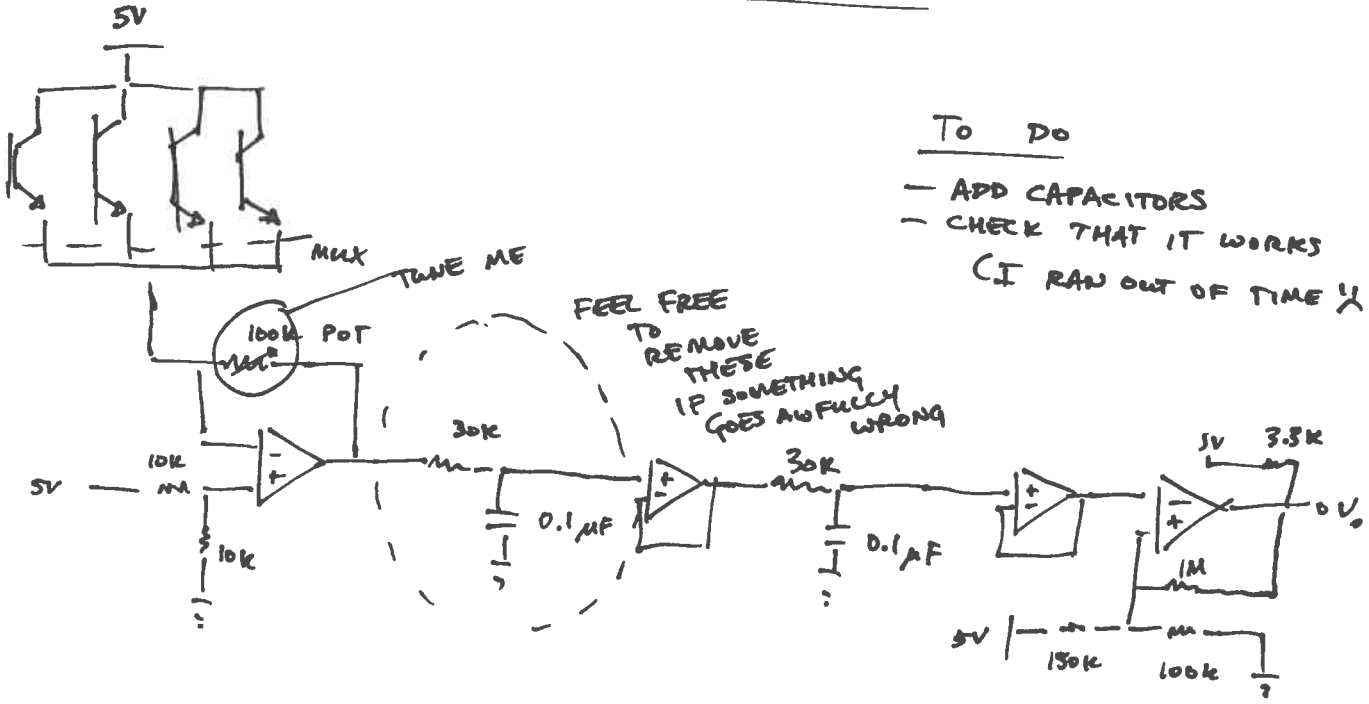


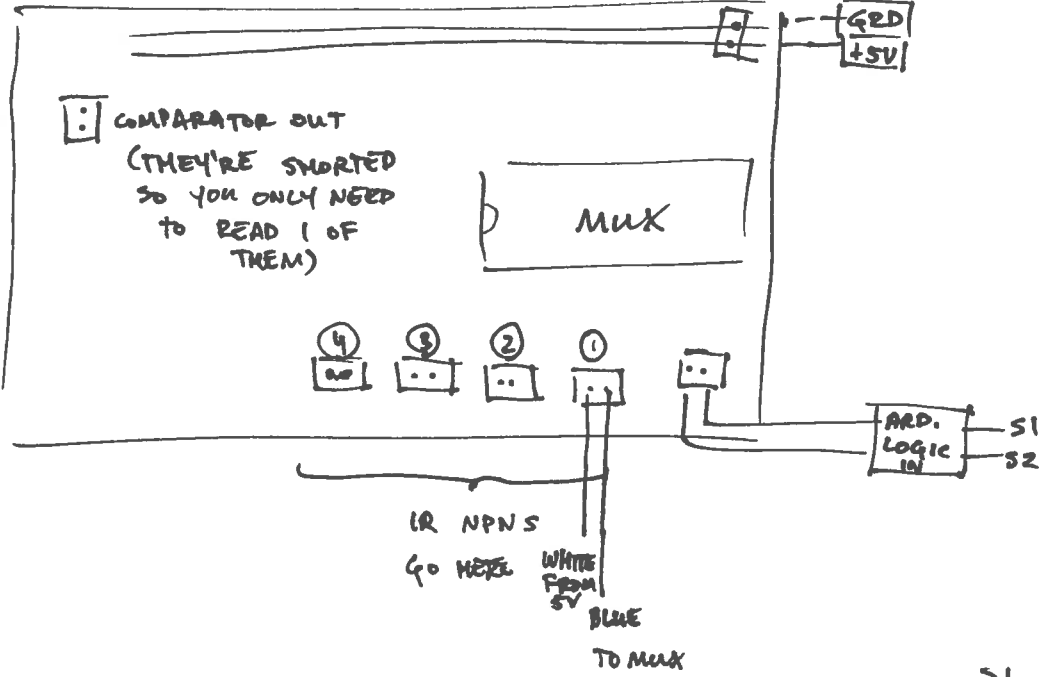
## To Do

- ADD CAPACITORS
  - CHECK THAT IT WORKS
- (I RAN OUT OF TIME :))


FEEL FREE TO REMOVE THESE IF SOMETHING GOES AWFULLY WRONG




S1	S2	MUX
0	0	#1
1	0	#2
0	1	#3
1	1	#4

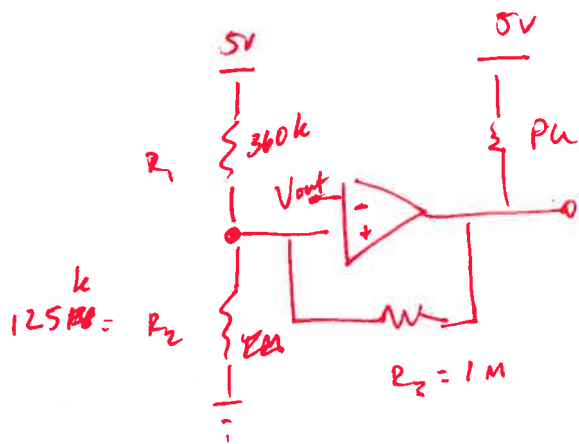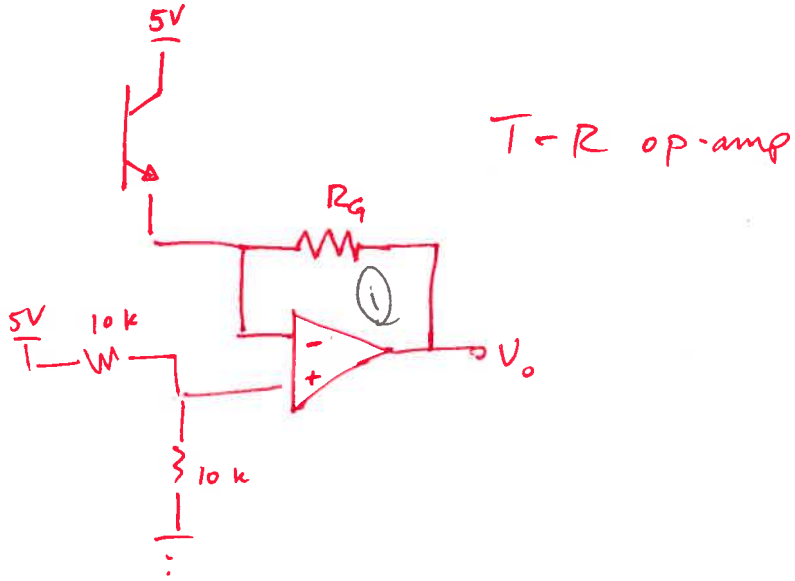


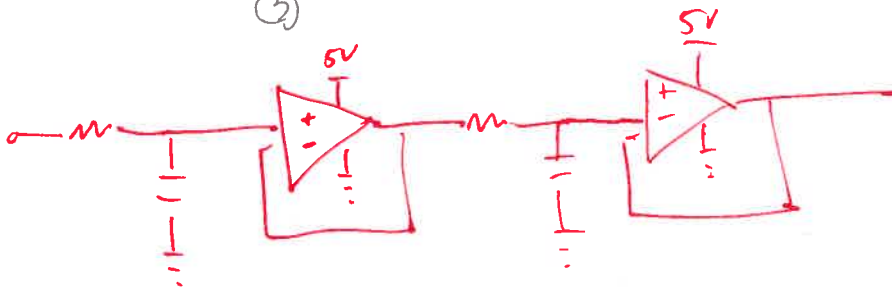- Parts
- 4 Op-Amps
  - 2 10k
  - 1 750  $\Omega$
  - 2 0.1  $\mu\text{F}$
  - 2 30k
  - 1 1M
  - 1 125k
  - 1 360k
  - 1 3  $\Omega$



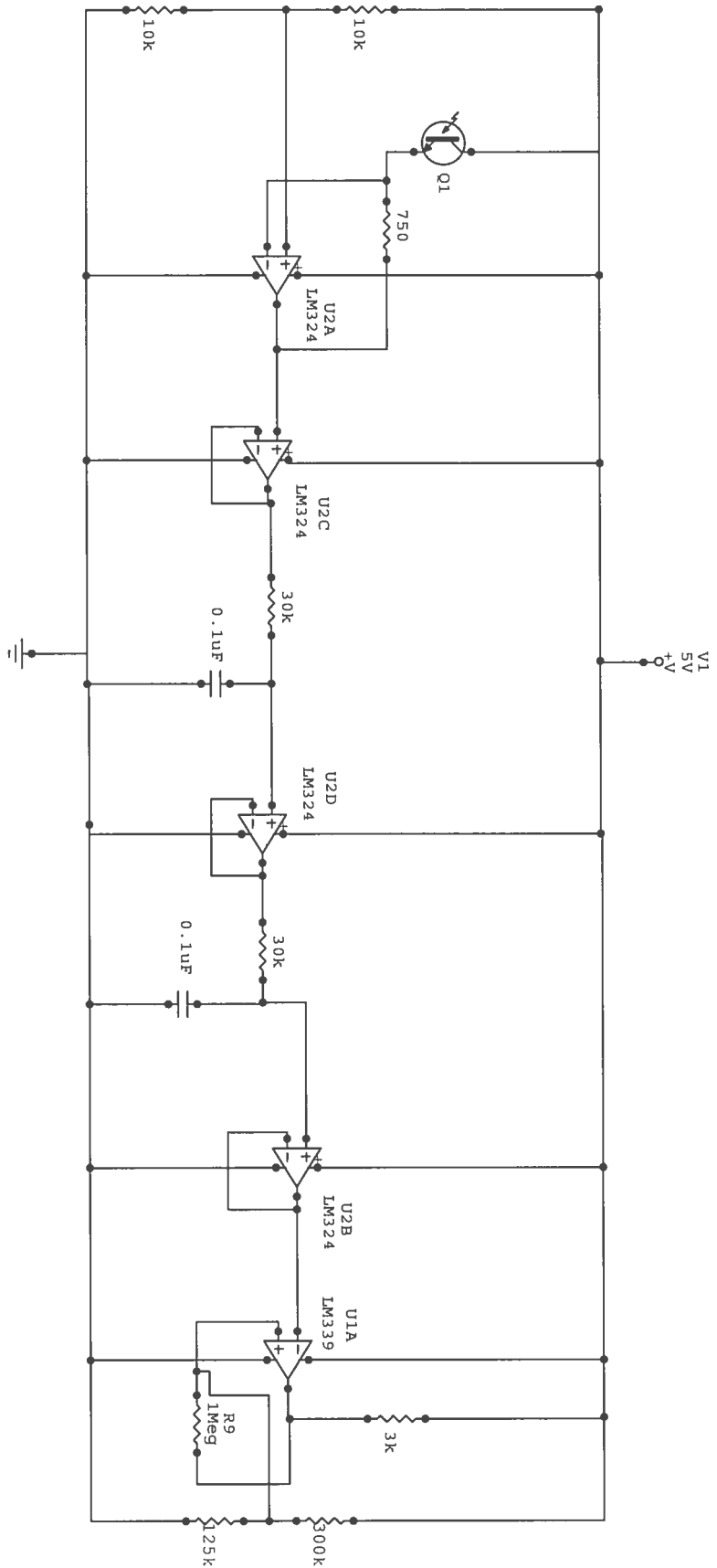

4000 Hz B.P.F

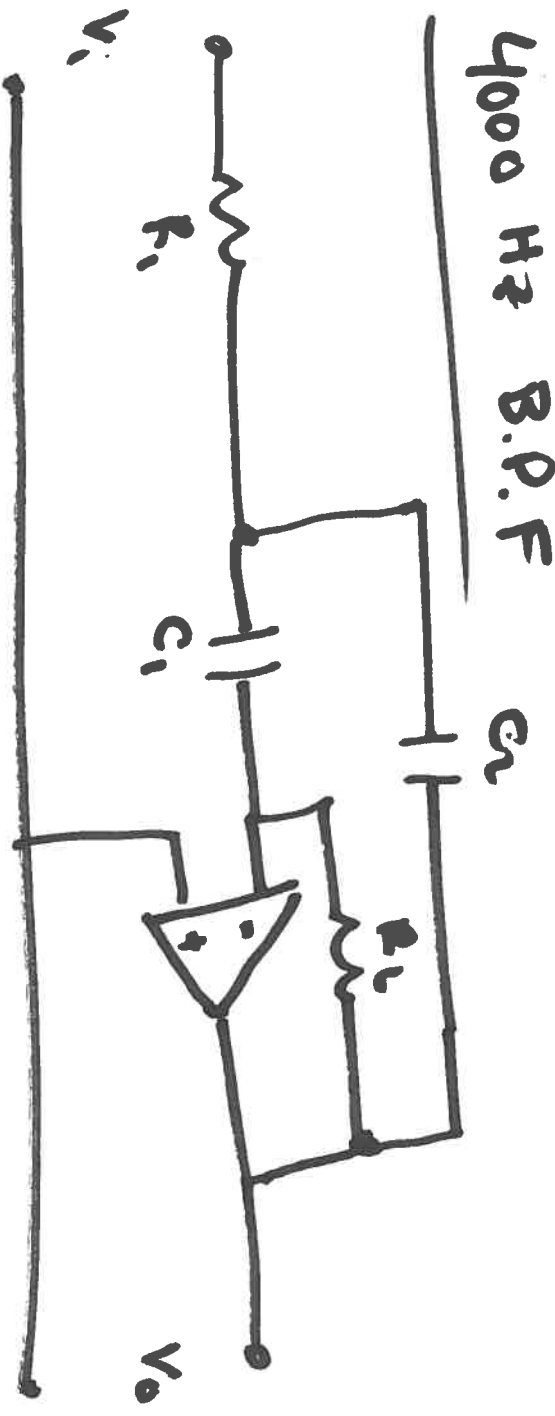

$$Q = \frac{1}{2} \sqrt{\frac{R_2}{R_1}}$$

$$f_v = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$Q = 5 = \frac{1}{2} \sqrt{R_2 / R_1} \implies \frac{R_2}{R_1} = 100$$

$$R_2 = 10k$$

$$R_1 = 1k$$

$$4000 = \frac{1}{2\pi \sqrt{10k^2 C_1 C_2}}$$


$$C_1 = .01 \mu F$$

$$C_1 C_2 = 1.58 \times 10^{-16}$$

$$C_2 \sim 1.5 \times 10^{-8} F$$



850 Hz B.P.F

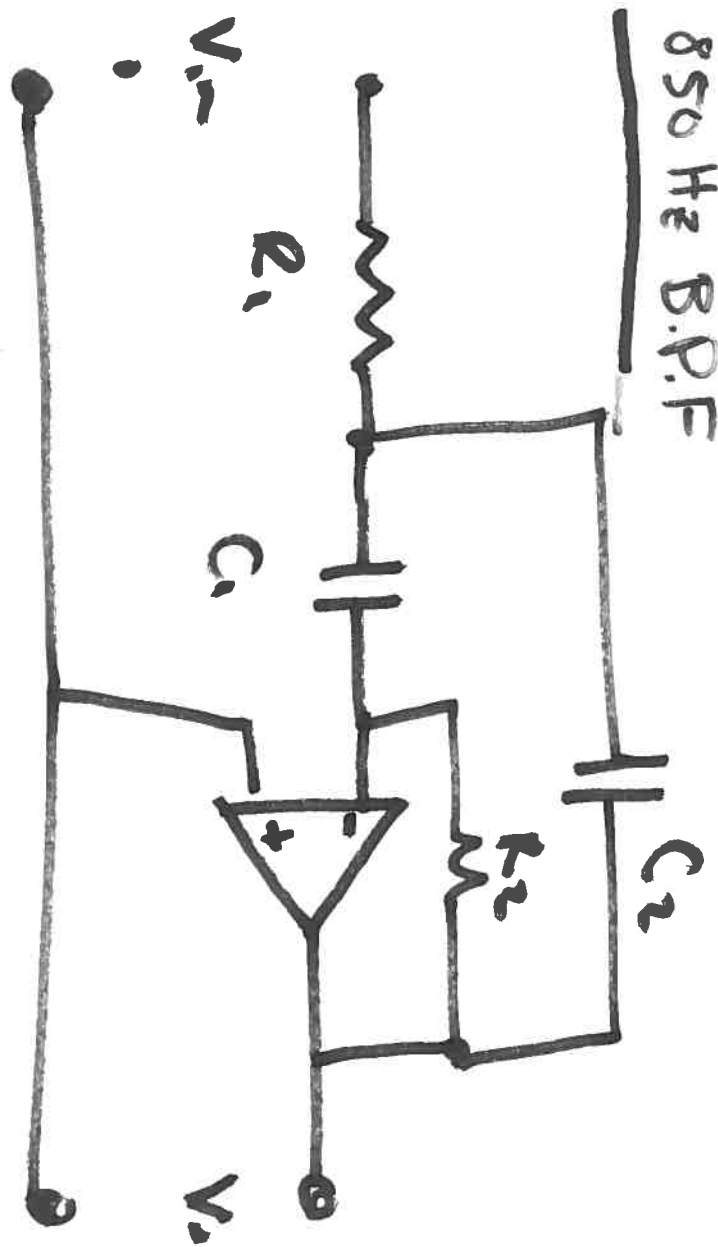

$$Q = \frac{1}{2} \sqrt{\frac{R_2}{R_1}}$$

$$f_v = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

So  $Q = 5 = \frac{1}{2} \sqrt{\frac{R_2}{R_1}} \Rightarrow \frac{R_2}{R_1} = 100$   $R_2 = 10k$   
 $R_1 = 1k$

$$850 = \frac{1}{2\pi \sqrt{10k \cdot C_1 C_2}} \quad C_1 = 0.1 \mu F$$

$$C_1 C_2 = 3.5 \times 10^{-16} \quad C_2 = 3.5 \times 10^{-8} \Rightarrow 47 e^{-8}$$


$$\sqrt{\quad} = 1.579 \times 10^{-4}$$

$$\xi = \frac{1.579 \times 10^{-4}}{C_2 (R_1 + R_2)}$$

$$C_2 = 0.1 \mu\text{F}$$

$$\xi = \frac{1.579}{R_1 + R_2}$$

$$R_1 + R_2 = 318 \Omega$$

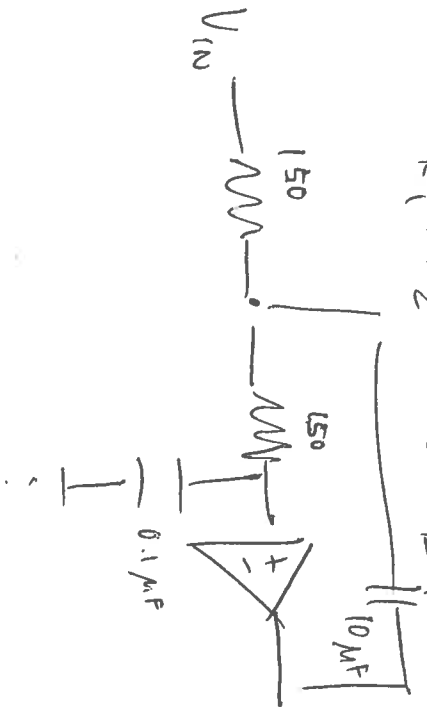

$$R_1 = 150$$

$$R_2 = 150$$

$$C_2 = 0.1 \mu\text{F}$$


$$C_1 = 1.1 \times 10^{-5}$$

$$= 11 \times 10^{-6} =$$

$$11 \mu\text{F}$$

$D = 5$   
 $C_1 = C_2 = 0.1 \mu F$   
 $R_1 = 10 k$   
 $f = 1000 Hz$   
 $4k f \sqrt{R_1 C^2} = \sqrt{R_2}$   
 $R_2 = 250$

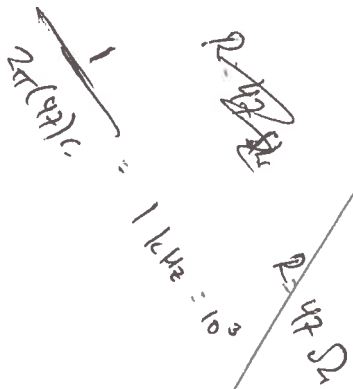$\frac{1}{2\pi RC} = 400 Hz$   
 $3.97 \times 10^{-8}$   
 $0.0397$



$3.3 \times 10^{-6} F$   
 $3.3 \mu F$



400 Hz  $\times 2$




Low Pass

$f_c = \frac{1}{2\pi RC} = 1 Hz$

$6\pi C = \frac{1}{RC}$



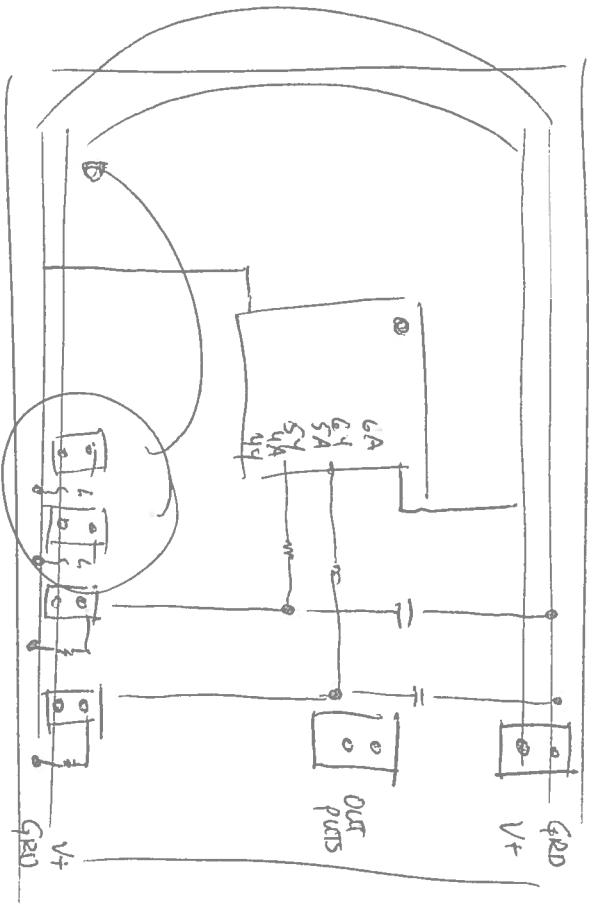


2 0.1 µF caps

2 100 k

2 10k


4 Molex

1 74HC14

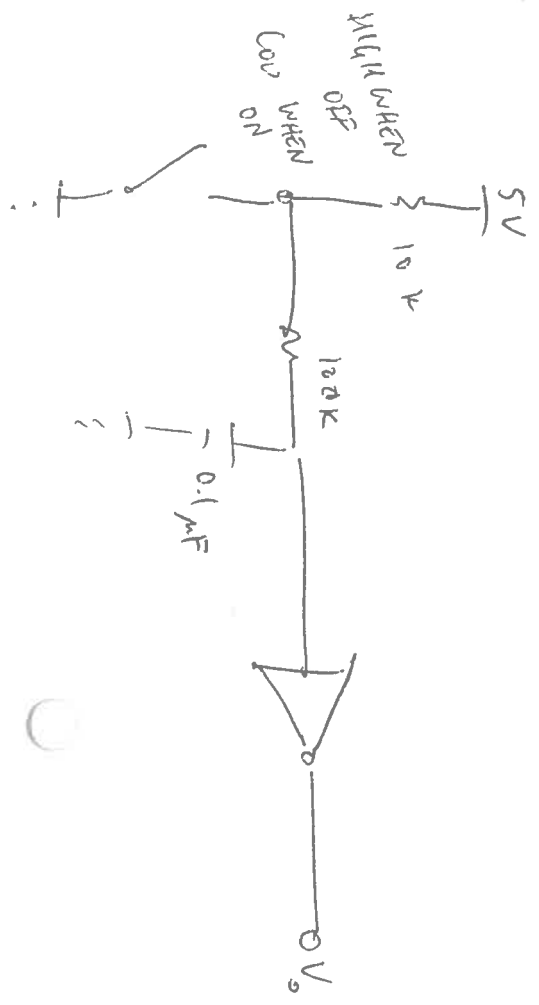

HIGH WHEN ON

LOW WHEN OFF

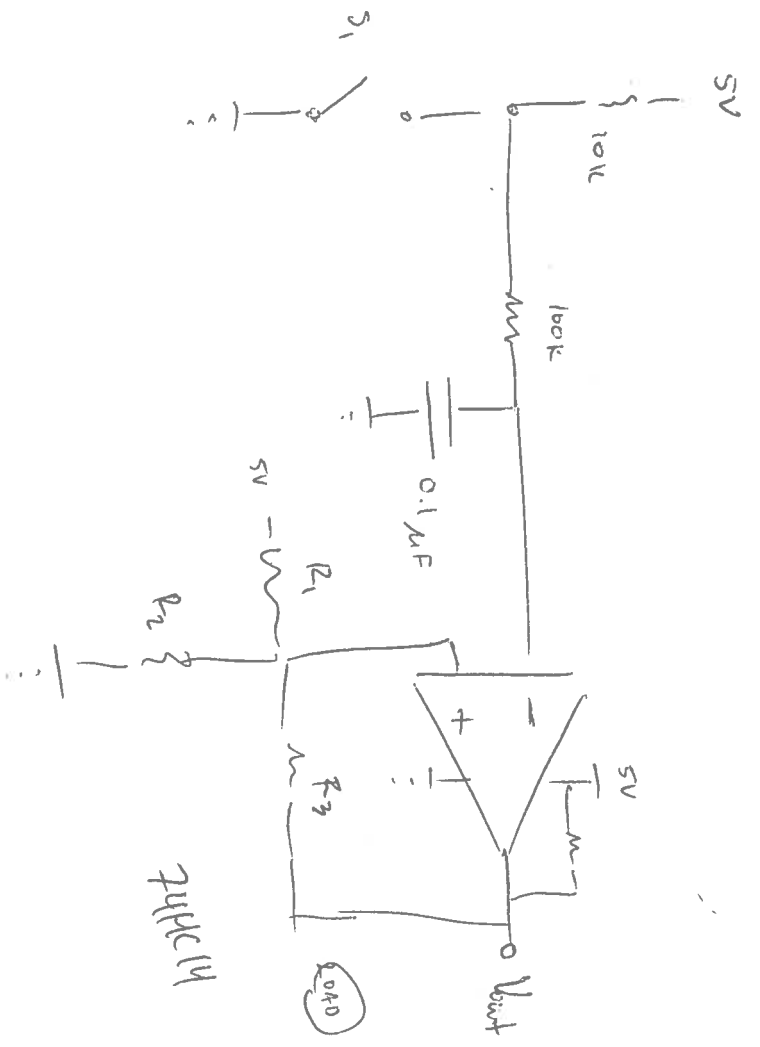

1A	6A	Vcc
14	6Y	
2A	5A	
24	5Y	
3A	4A	
34	4Y	
4		



~~V<sub>A</sub> = 2V~~  
~~V<sub>B</sub> = 3V~~

V<sub>A1</sub> = 3V

V<sub>A2</sub> = 2V

ΔV = 1.0V

$\mu = \frac{\Delta V}{V_{A2}} = 0.5$

R<sub>g</sub> = 1 MΩ

R<sub>e1</sub> = 500 kΩ

$R_1 || R_3 = \frac{1}{\frac{1}{15} + \frac{1}{1}} = 333 \text{ k}\Omega$

R<sub>2</sub> = 333


TO ADDRESS


STATE DIAGRAM

— How to Tell if we have Forward

— How to Tell if we're outside circle


— REMOVE CASTLE

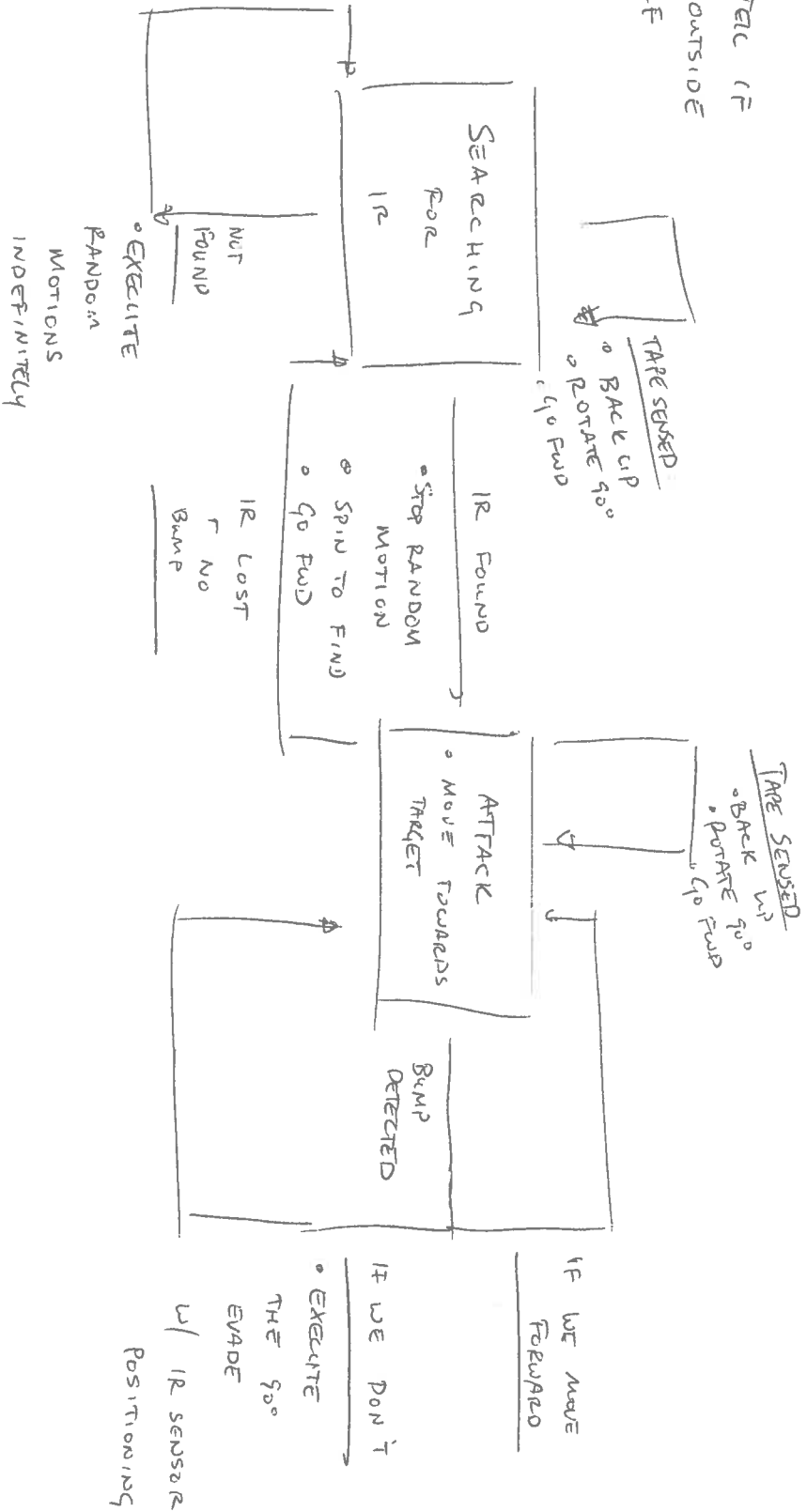

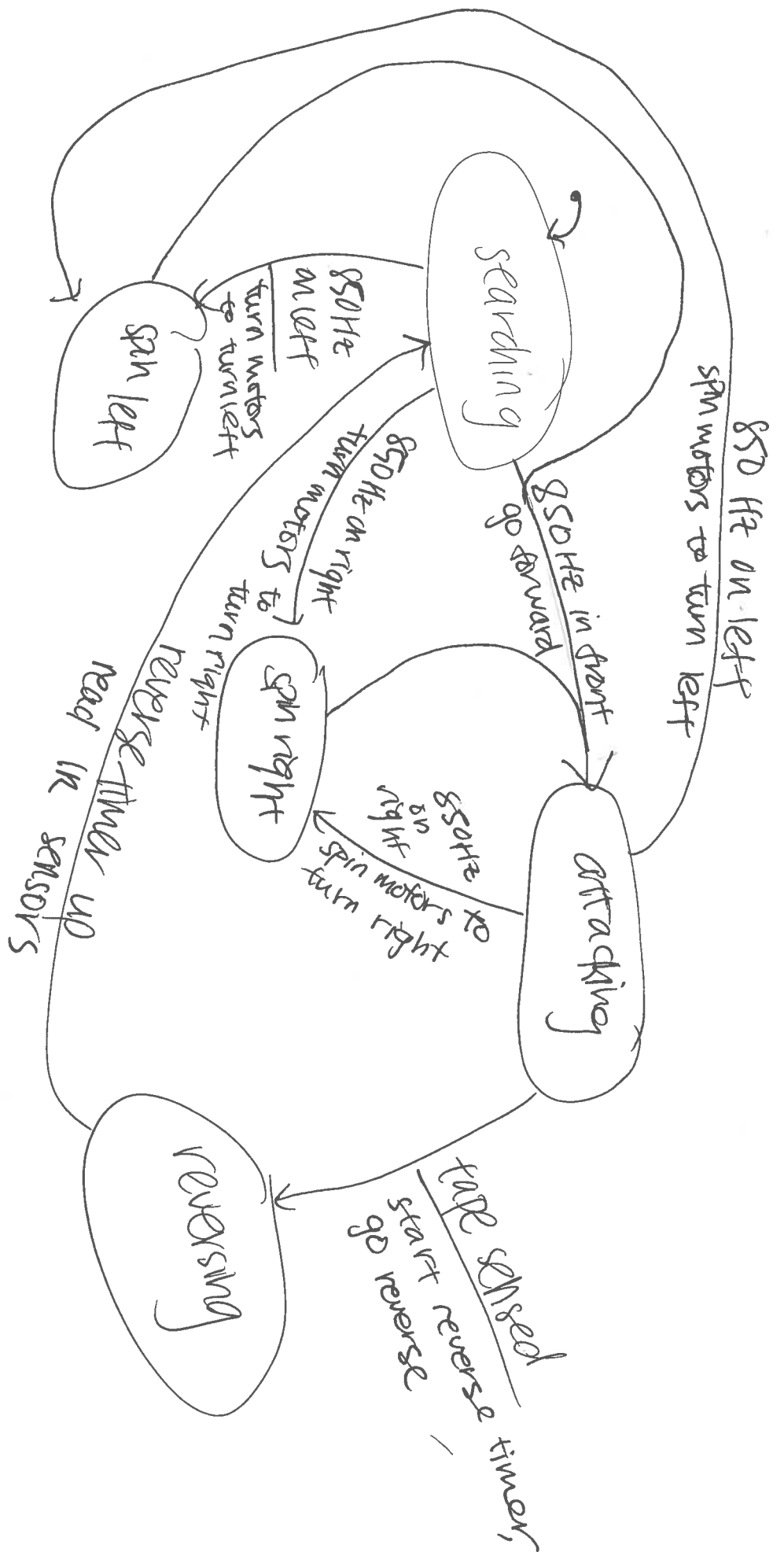

brick code

3/5/13

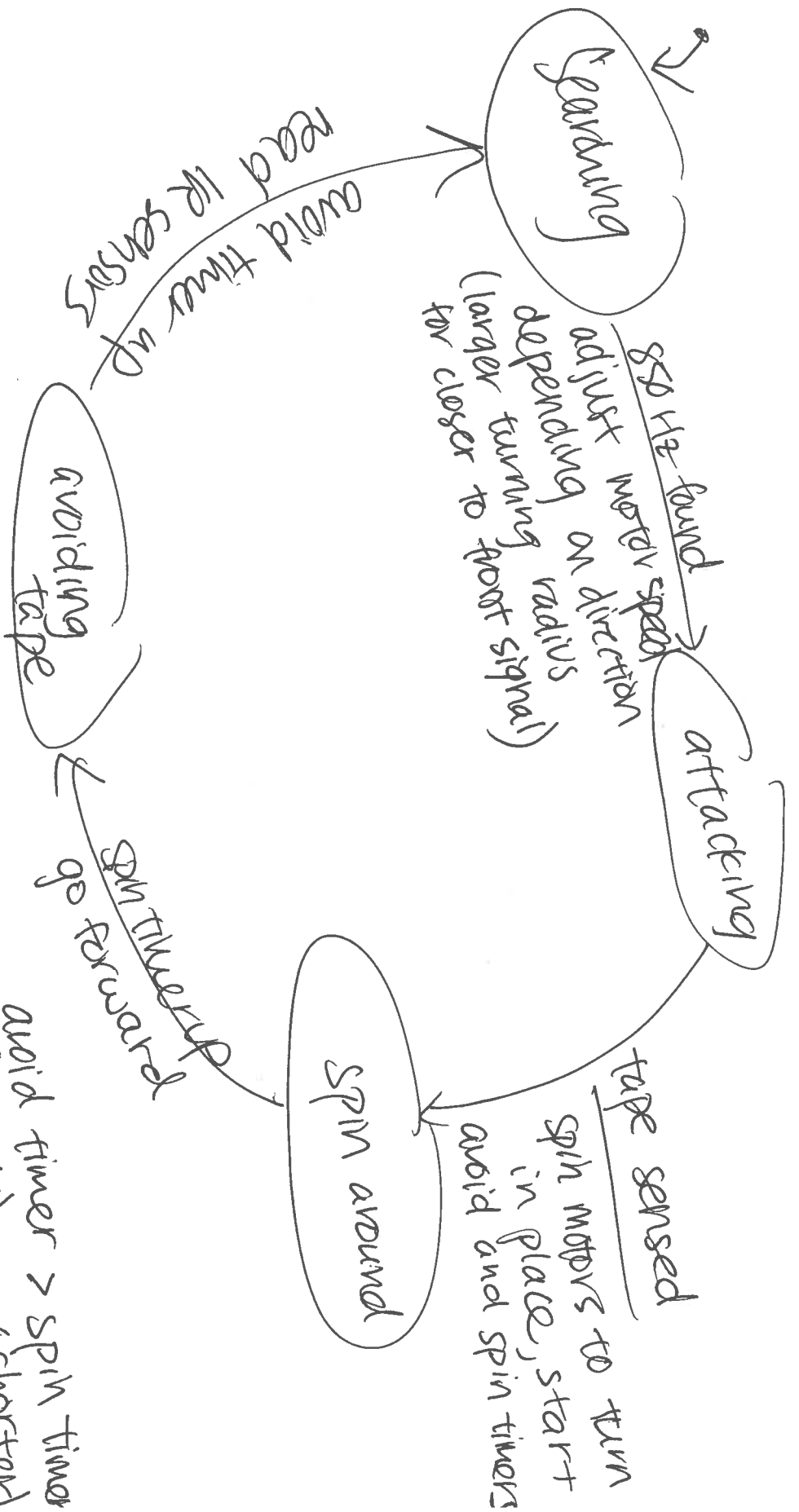


avoid timer > spin timer  
(longer) (shorter)

brick code

3/3/13



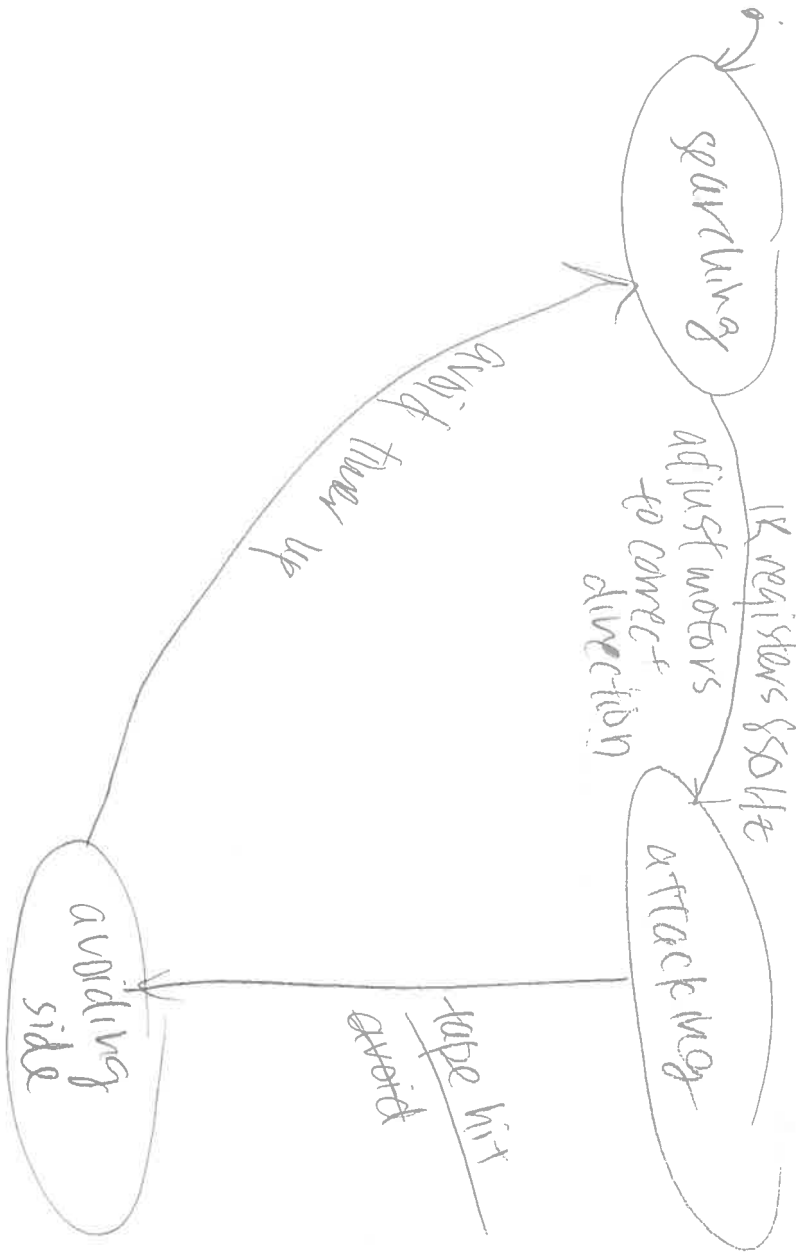

a)

Header

Navigation

Content

b)

Header

tab Navigation

Content

Content

Content

Footer

Header

Content

Content


img link

img link

Content

c)

# System Integration

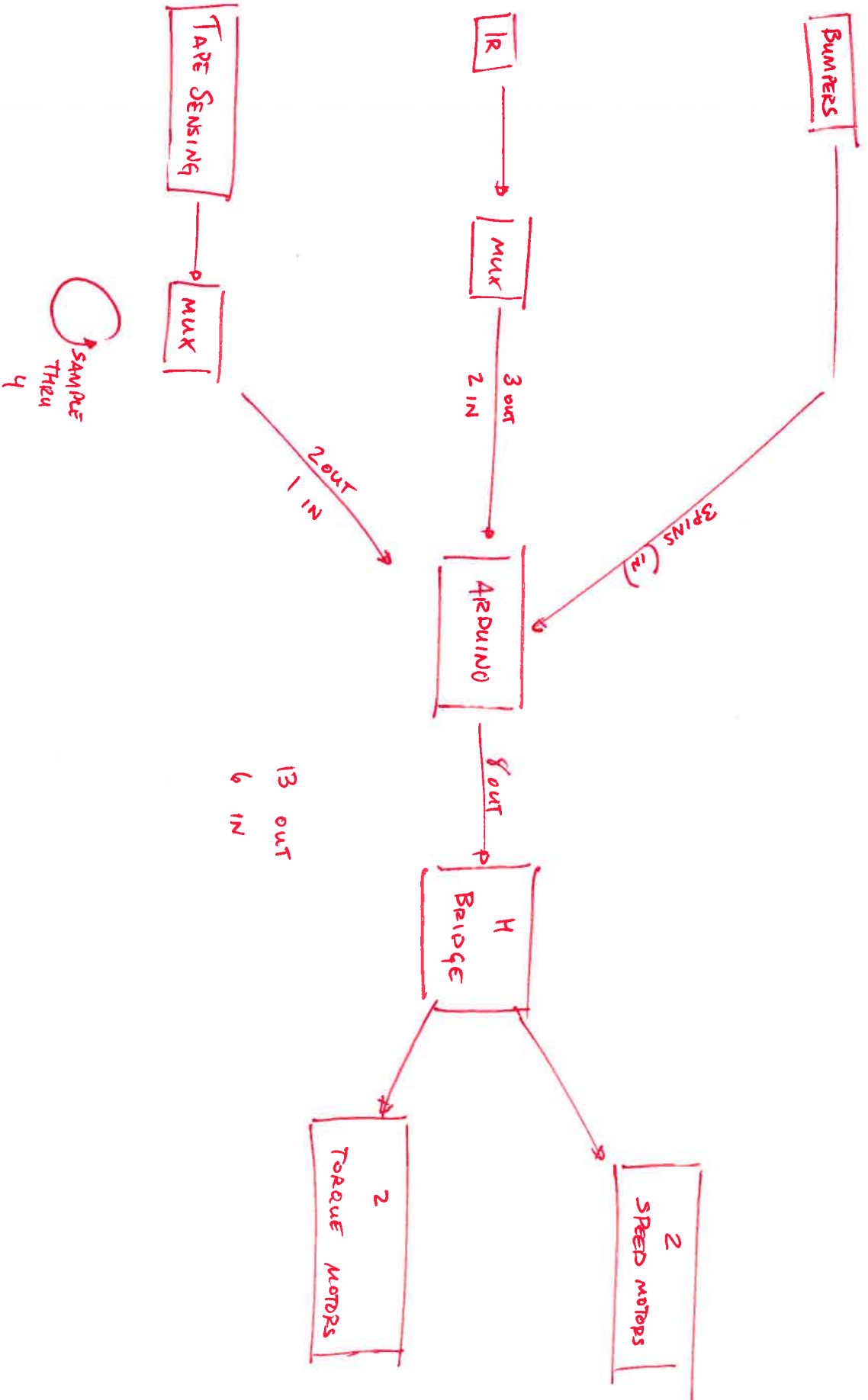

# Top View



non-bumper


Front



3 1/2




3 1/2

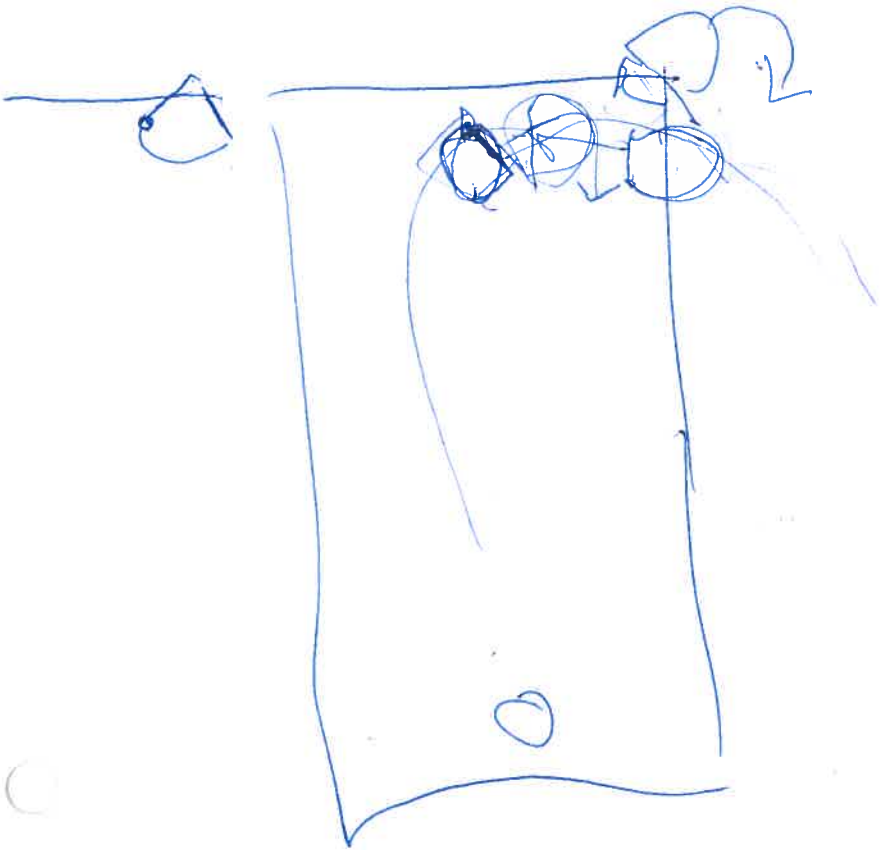

2/18/13


# Uses for Bump Sensing

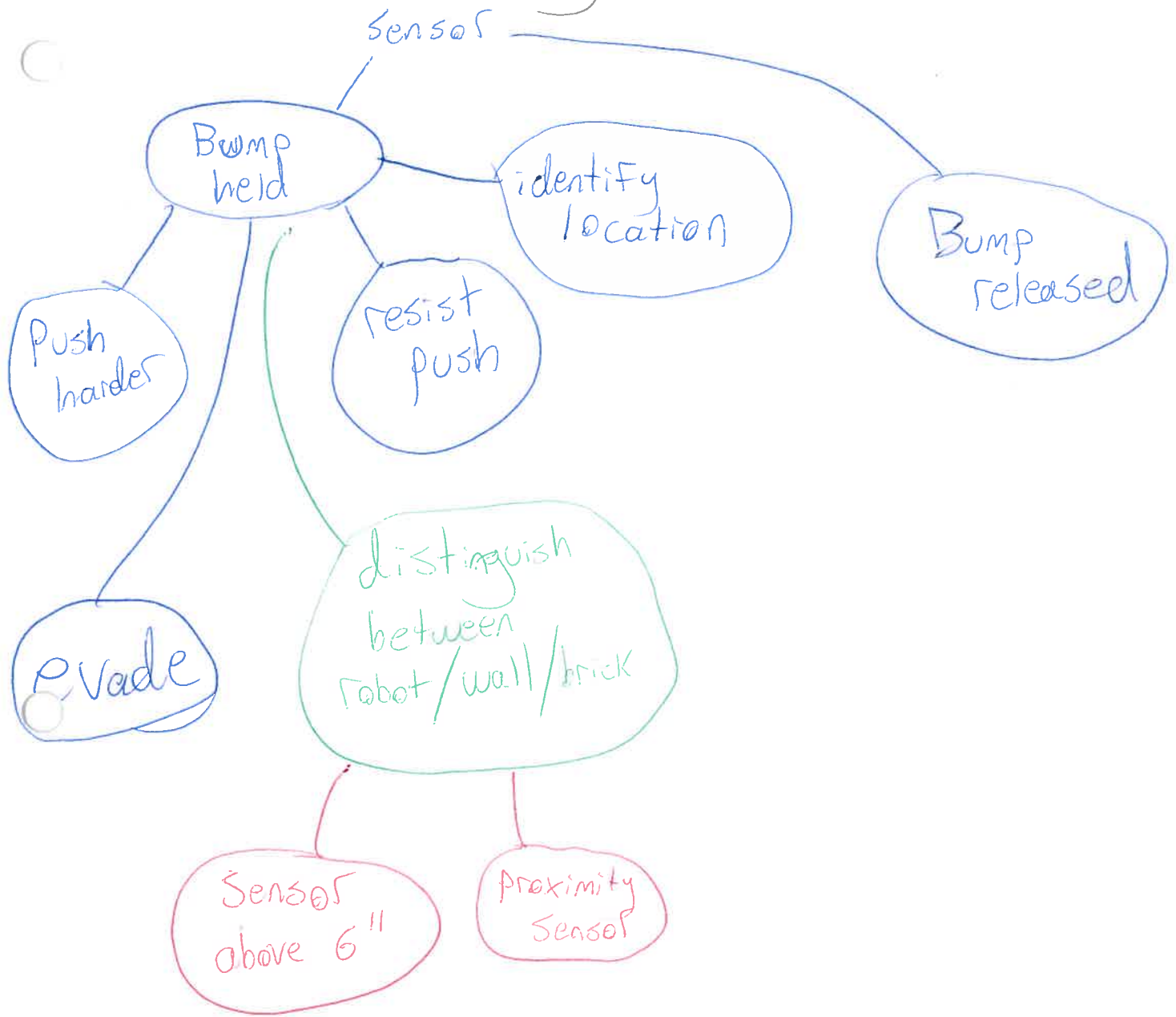


# Bumper Sensors

Mechanical Switches

home made

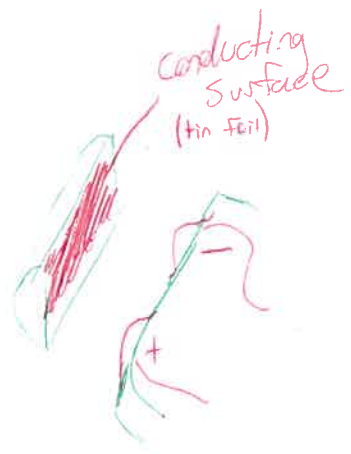


bump switch

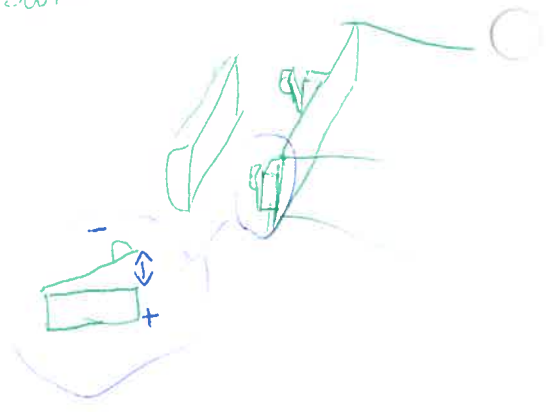

# Debounce Techniques

## Hardware

see textbook 283-284

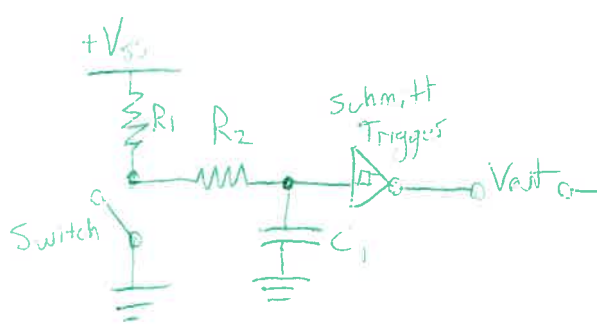

$V_{SS} \approx 1.1 \cdot V_{IH}$  For Arduino  
 $R_1 \approx 10 \text{ k}\Omega$  - much smaller than Arduino impedance  
 $\tau = R_2 \cdot C_1$  ← Switch bounce time (order of 10 ms)

Chip LM339 Comparator w/  
 $V_{ref} > V_{out}$  at time  $\tau$   
 74HC14 Inverter w/ Schmitt Trigger

## Software


$\tau =$  switch bounce time

```

Test For Switch
  if switch changed && (CurrentTime - lastSwitchTime > 10  $\tau$ )
    Flip Switch var
    lastSwitchTime = currentTime CurrentTime
  end
  CurrentTime = Get Time()
    
```

Circle

Fully maneuverable  
360°

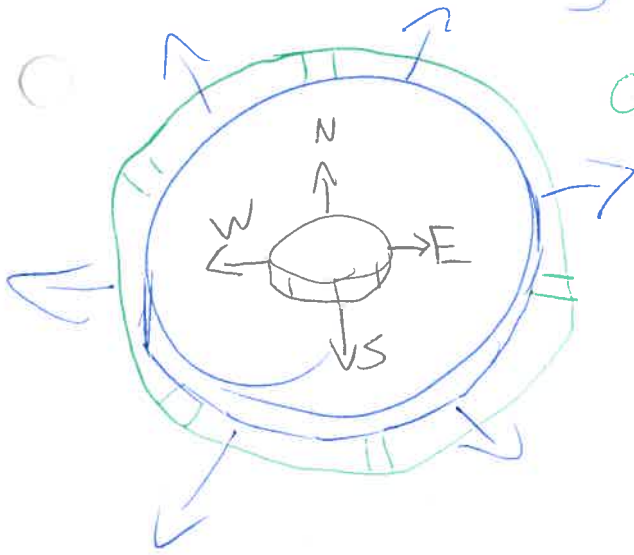


Can bump/push in any direction  
- no need to rotate

# State Diagram


2/19/13

Start initialization

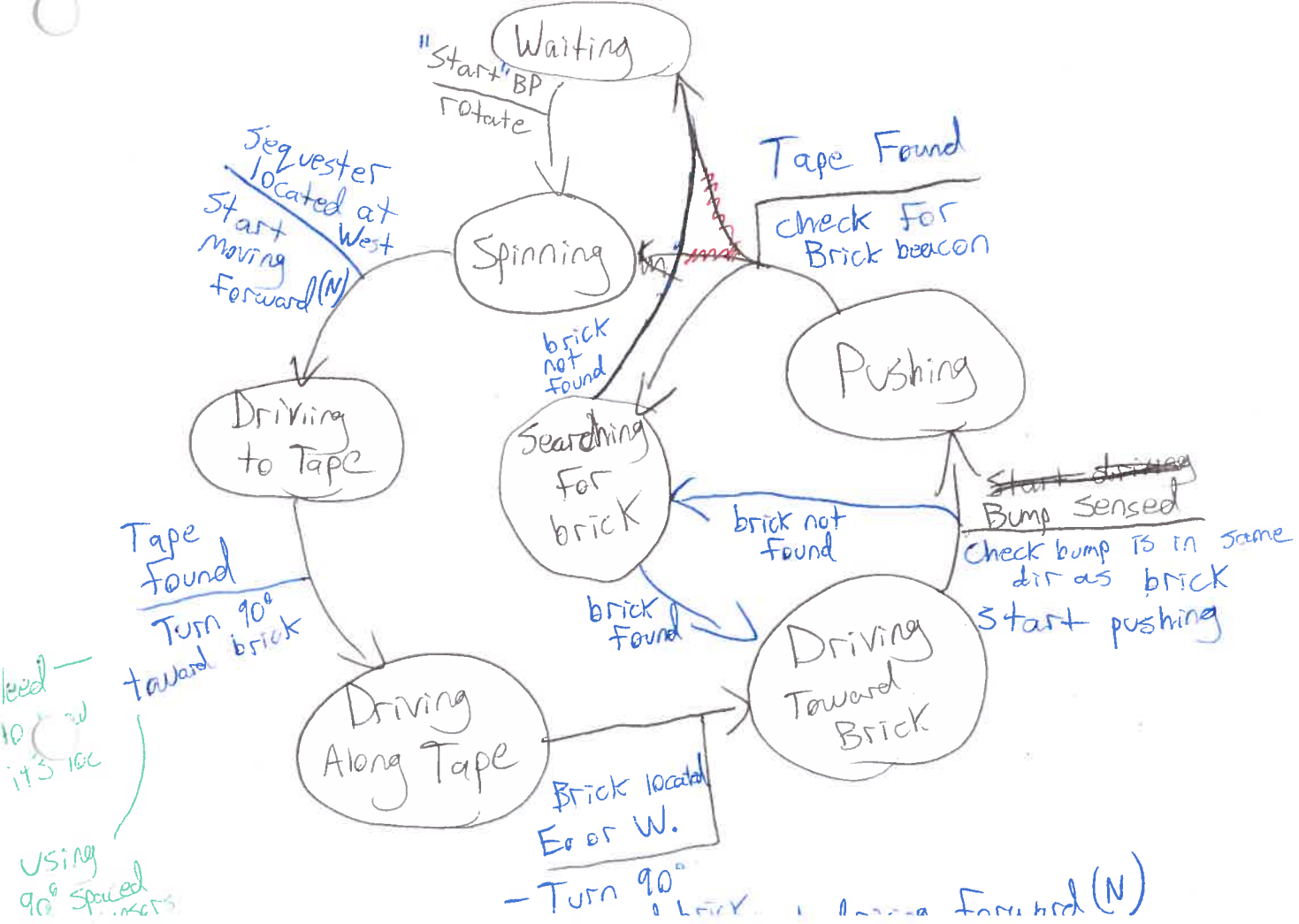


lead to its loc  
using 90° spaced

- Turn 90° ... Forward (N)

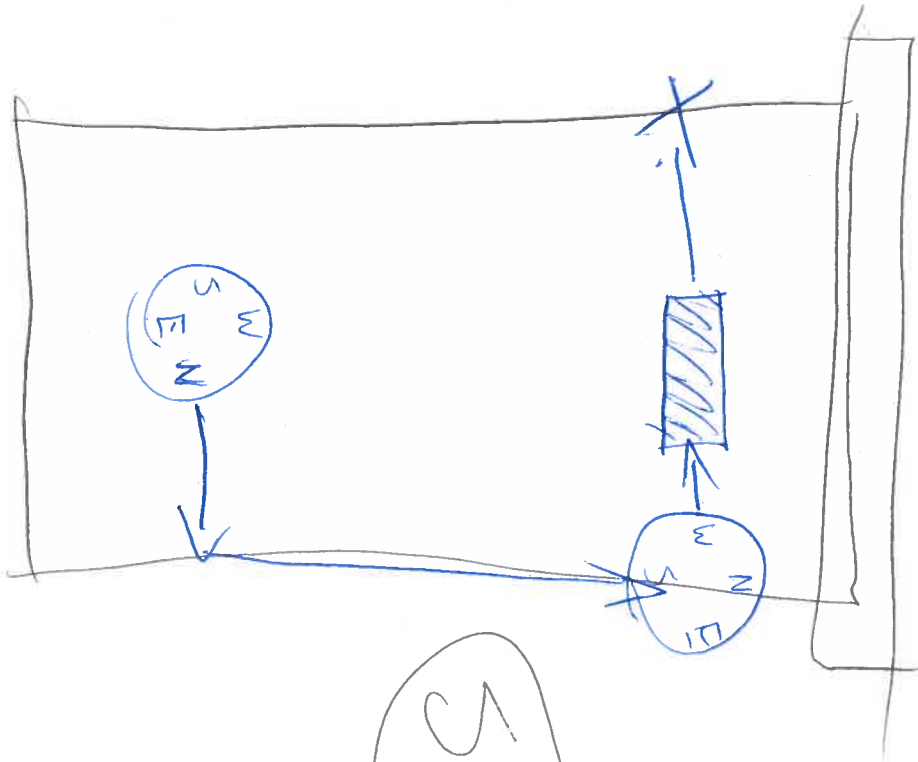



Strategies

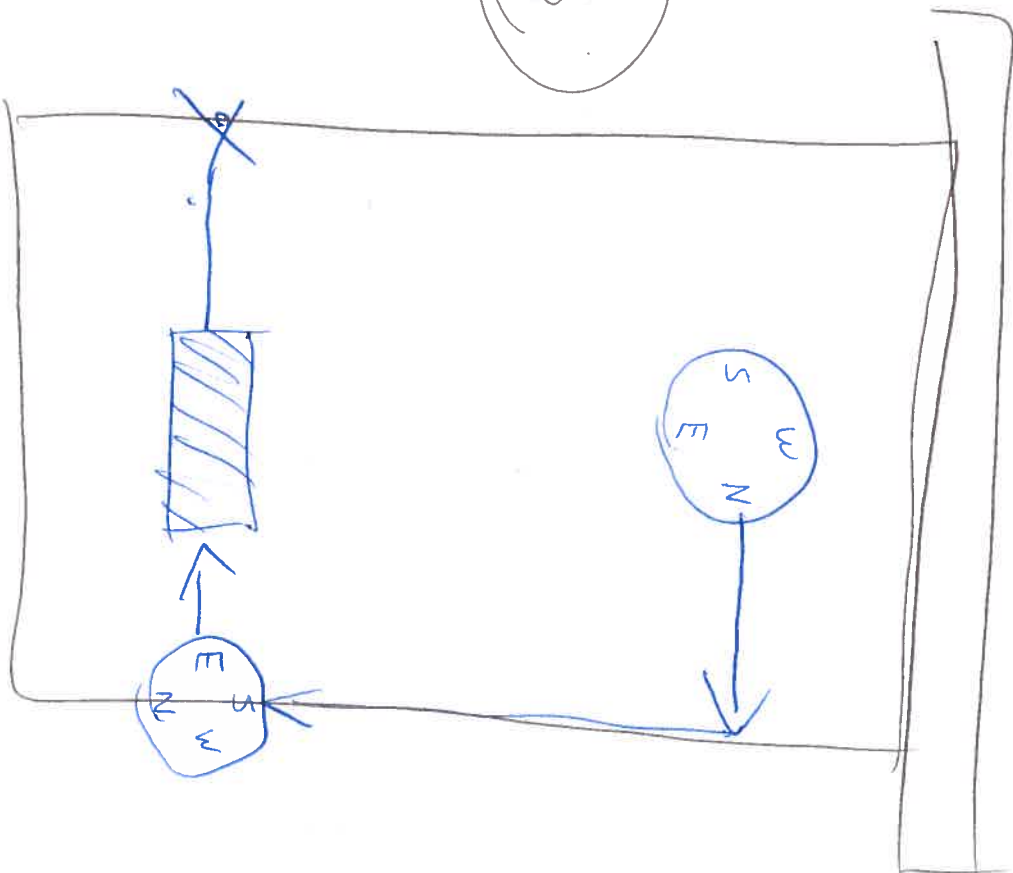




# Front Bumper Array

2/21/13

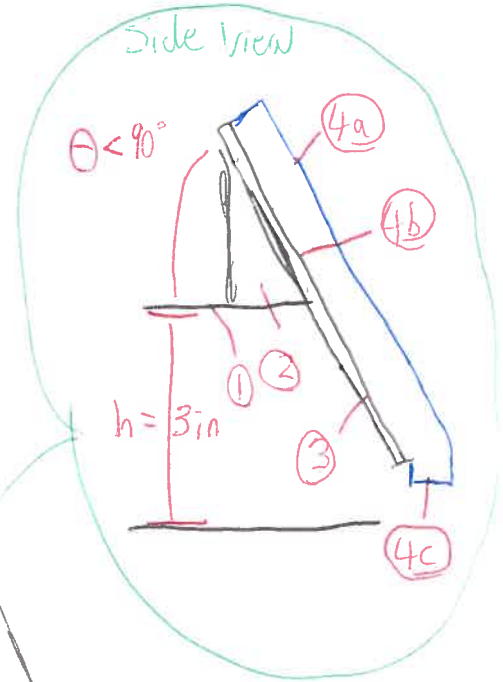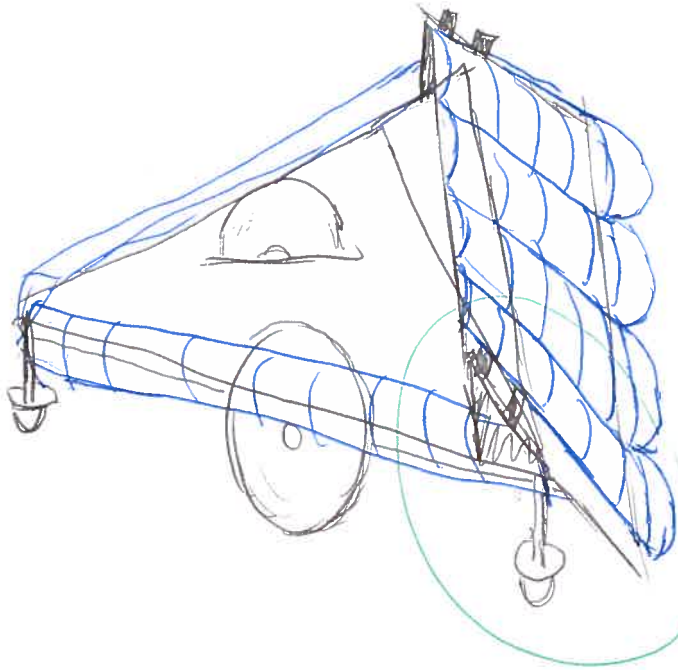



- ① bot platform
- ② bumper support  
- determines bumper angle (possibly adjustable)
- ③ bumper bed (grounded contact surface)
- ④a bumper foam (flexible)
- ④b inner surface of bumper held at high voltage
- ④c inner bumper switch specifically designed for wall bumps

## Switch Design

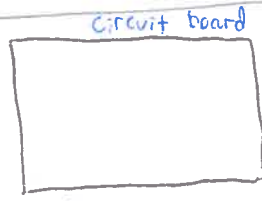

bumper bed



③

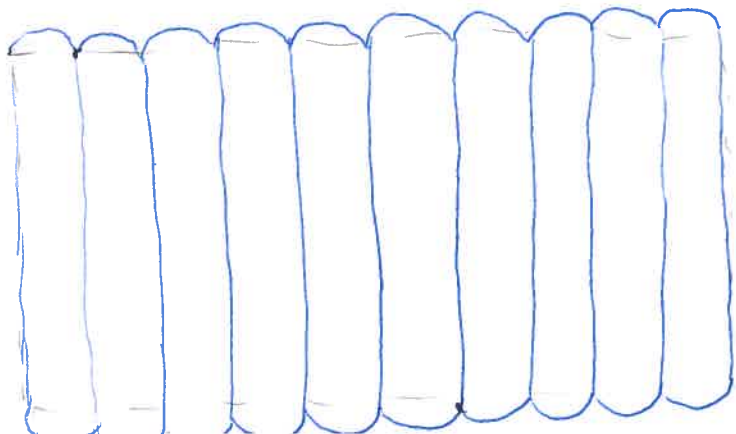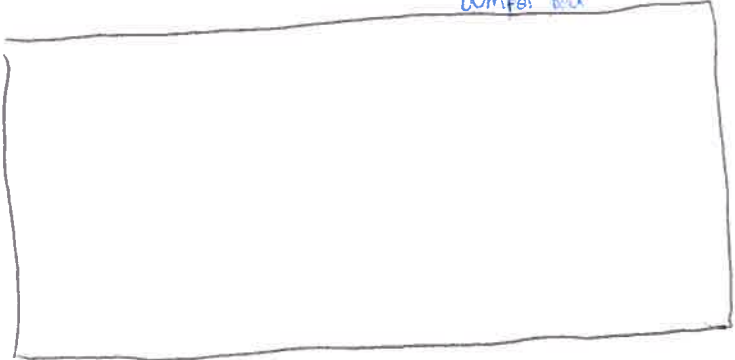

bumper foam (lays on top of bumper bed)

④a-c



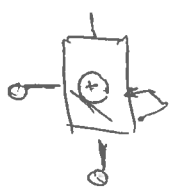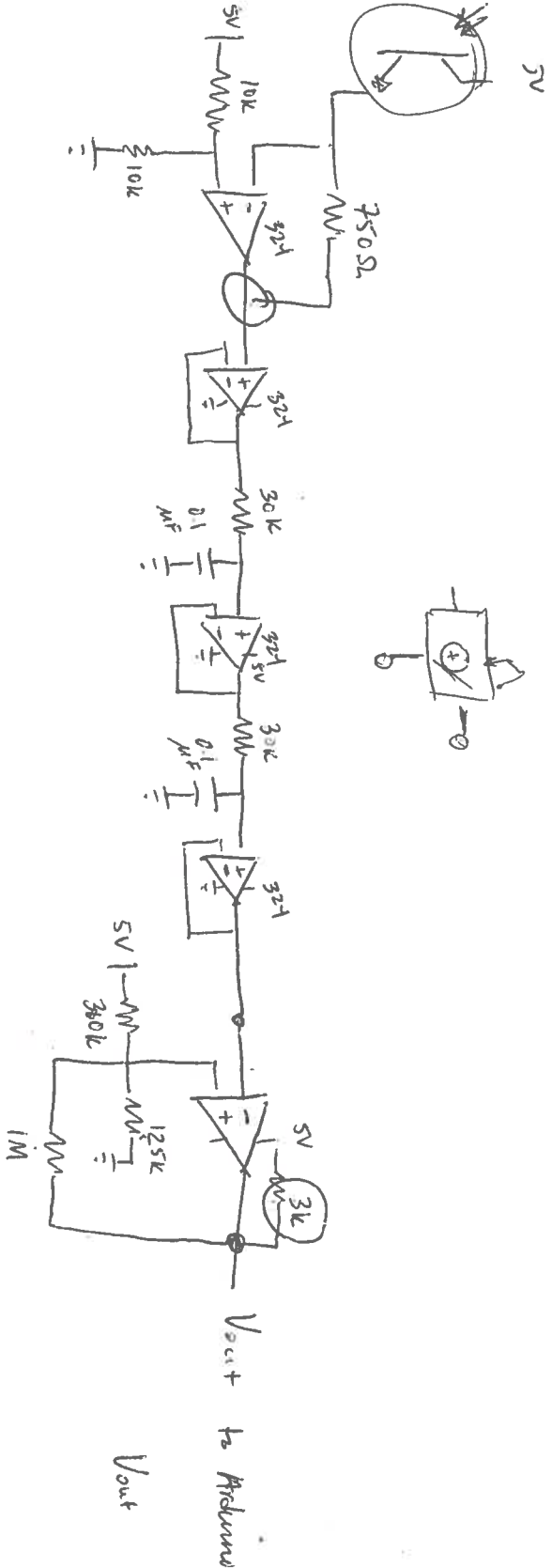

TEST INFO:



$\Delta V \approx 0$  for black

$\Delta V \approx 0.50V$  to  $0.01V$   $\therefore I$  is ranging from  $\frac{\Delta V}{R} = 0.013mA$  to  $0.667mA$

we'd like  $0.667mA$  to map to  $0.5V$ ,  $R = \frac{\Delta V}{I} = 3k\Omega$ ?

$0.020mA$  to map to  $0.5V$ ,  $R = 25k\Omega$   $100k\Omega$

$$V_{A1} = 2.0$$

$$V_{A2} = 1.7$$

$$n = \frac{0.3V}{1.7V} = 0.176$$

$$R_{out} = 3k\Omega$$

$$R_3 = 1M\Omega$$

$$R_1 = nR_3 = 176k\Omega$$

$$R_2 = \frac{R_1 \parallel R_3}{\frac{5V}{2V} - 1} = 100k\Omega$$





$$R_3 = 100k$$


$$R_1 = 176k\Omega$$

$$R_2 = 10k\Omega$$

$$V_{out} = (V_{cc} - V_{ref}) \frac{R_3}{R_{pu} + R_3}$$

$$(5 - 1.6) = 3.4 \text{ high}$$

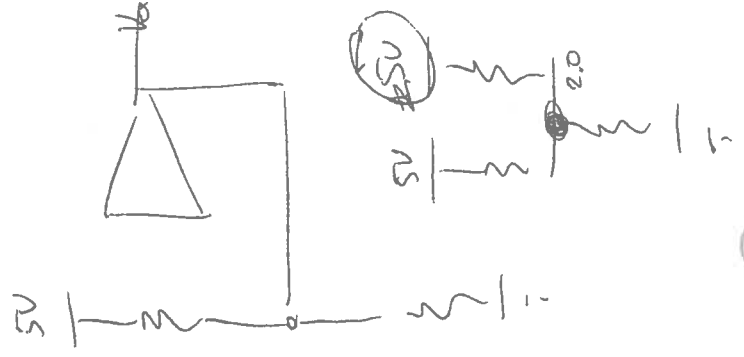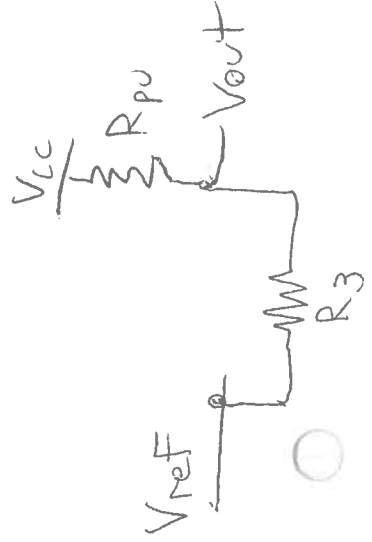

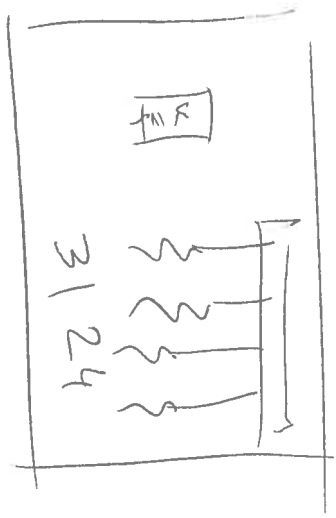

◦ 90° EVADE STRATEGY

◦ RANDOM CONFUSED STATE

◦ BUMP SENSORS




◦ TELL IF


WE'RE

~~THE~~ MOVING

FORWARD

—

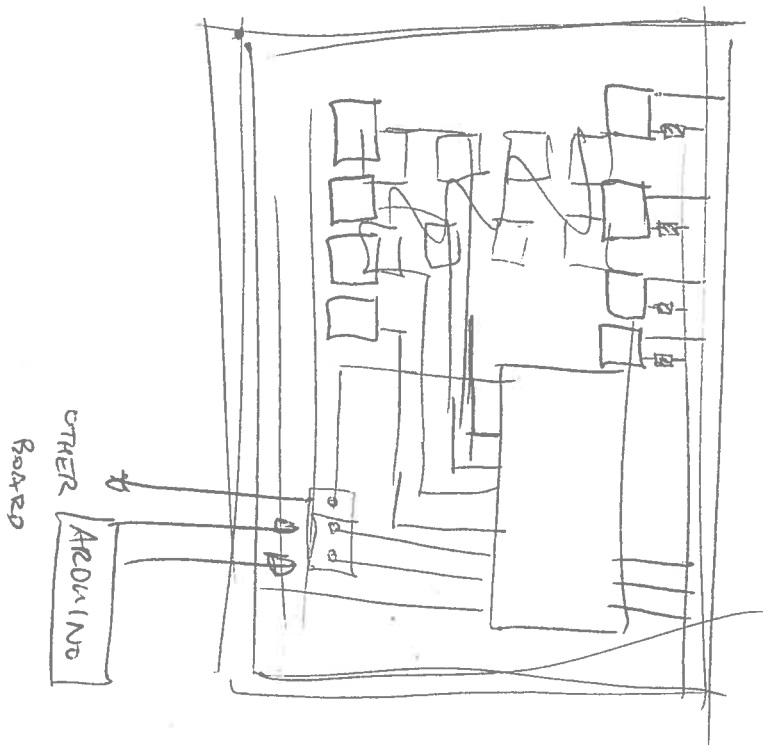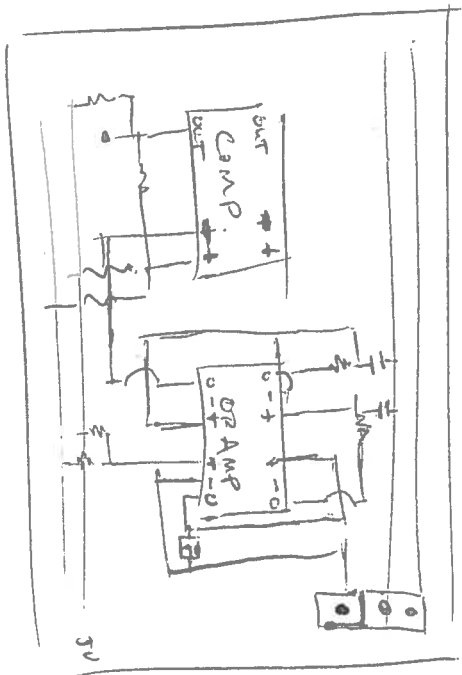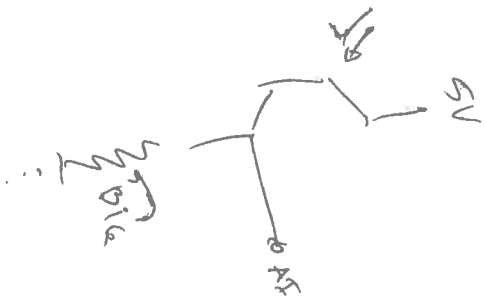

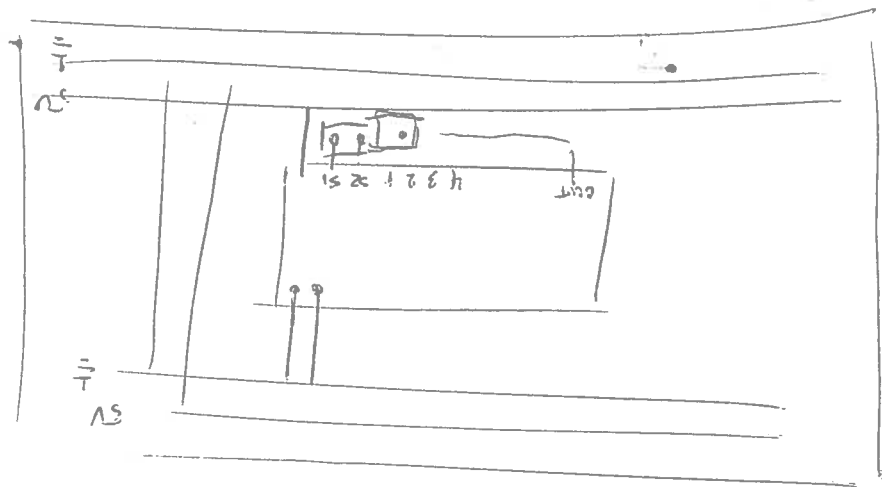



200 mV but need  $\geq$  500mV

$$V_{A_1} = 600\text{mV}$$

$$V_{A_2} = 400\text{mV}$$

$$n = \frac{200}{400} = \frac{1}{2} \quad R_3 = 1\text{M}\Omega$$

$$R_1 = \frac{1}{2}\text{M}\Omega$$

$$R_2 = \frac{.33\text{M}\Omega}{\frac{5}{.6} - 1} \rightarrow R_2 = 45\text{k}$$

~~$V_{A_1} = 650$~~

~~$V_{A_2} = 450$~~

~~$n = \frac{200}{450} = .444$~~

~~$R_1 = 74\text{M}\Omega$~~


~~$V_{A_1} = 750$~~

~~$V_{A_2} = 650$~~

~~$n = \frac{200}{650} = .307$~~

$$R_1 = 33\text{k}$$

$$R_2 = 4.7\text{k}$$

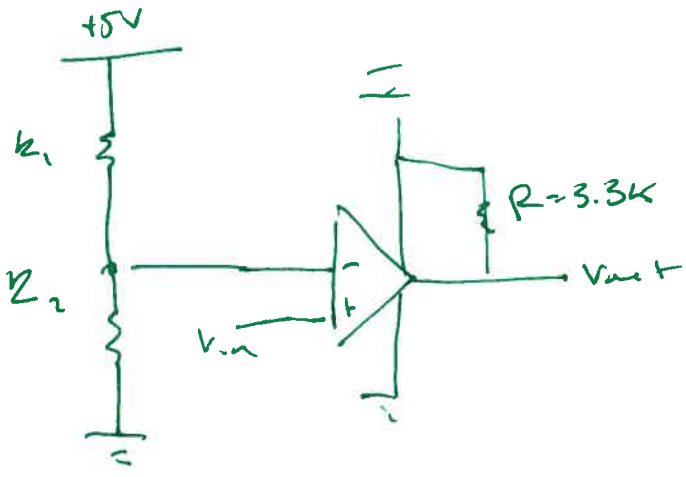

I want  $V_{out}$  to be 200 mV

$$\left( \frac{R_2}{R_1 + R_2} \right) 5 = .2$$

$$\frac{R_2}{R_1 + R_2} = .04 \rightarrow \frac{25}{25} = \frac{R_1}{R_2} + 1 \quad \frac{R_1}{R_2} = 24$$

~~$R_1 = 24k$~~   $R_1 = 24k$   
 ~~$R_2 = 1k$~~   $R_2 = 1k$


GAIN

$$\left( \frac{R_2}{R_1 + R_2} \right) 5 = .6$$

$$\frac{R_1}{R_2} + 1 = 8.33$$

$$\frac{R_1}{R_2} = 7.33$$


$R_1 = 6.8k$   
 $R_2 = 1k$

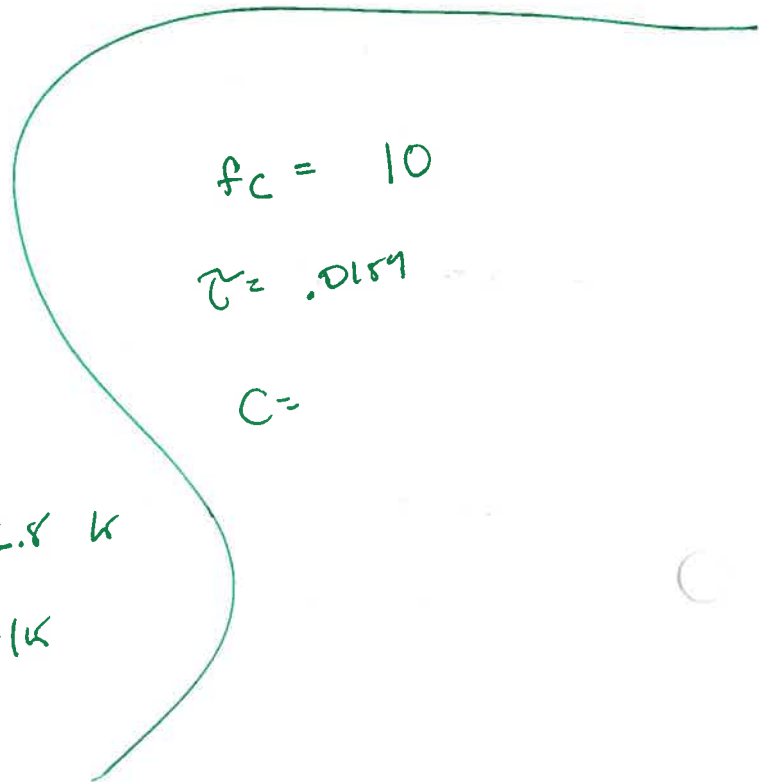

$$R = \frac{V}{I} = \frac{100\text{mV}}{5\text{mA}} = 20$$

$$2.5\text{V}/R = 5\text{mA}$$
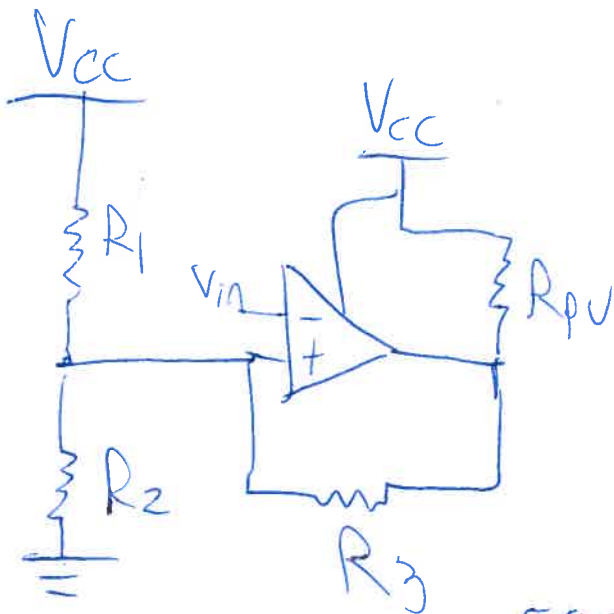
$$V = IR \quad R = \frac{100\text{mV}}{3\text{mA}} = 33$$



$$R_{pu} = 3.3\text{V}$$


$$R_3 = 1\text{M}\Omega$$

$$R_1 = n R_3 = 1\text{M}\Omega$$

$$R_2 = \frac{500\text{k}}{\frac{5}{.05} - 1} = 6.1\text{k}$$

Threshold  $VA_1 = 60\text{mV}$  ~~50mV~~  
 to be high  $10\text{mV}$   
 $5\text{mV}$   
 to go low  $VA_2 = 30\text{mV}$  ~~30mV~~ ~~30mV~~

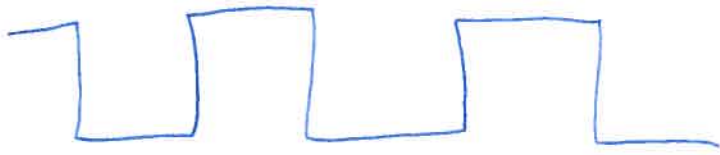
$$n = \frac{\Delta VA}{VA_2} = \frac{30}{30} - 1$$




light



sensor

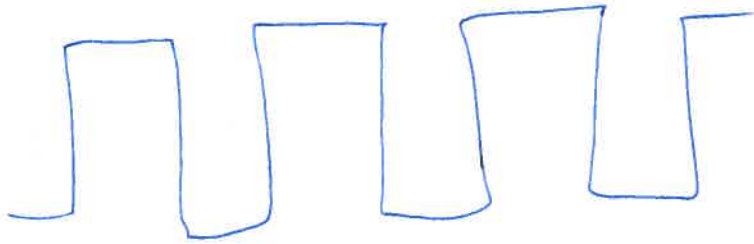


w/  
gain

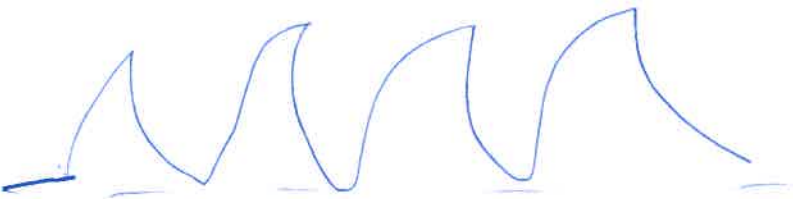



850 kHz




4 kHz

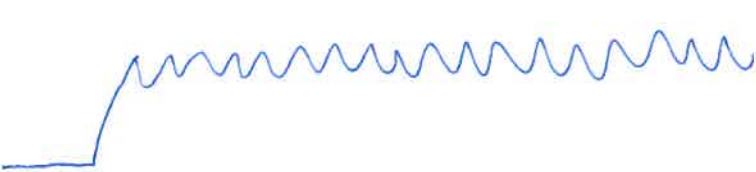

4 kHz  
to  
DC

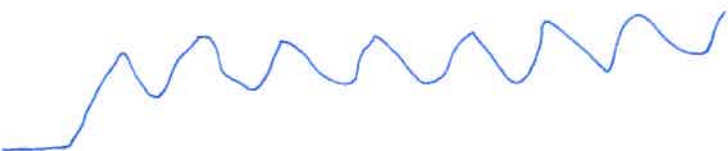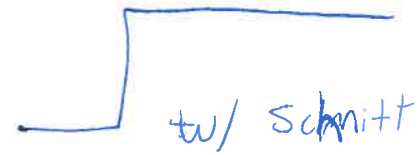

850 Hz  
to  
DC

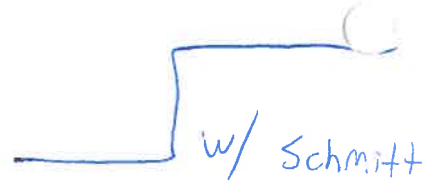

# high pass design

# Sequester Beacon Sensing

want 850 Hz to be attenuated  $\sim .001$

use ~~low~~ high pass filter

$$\frac{\omega \tau}{(1 + \tau^2 \omega^2)^{1/2}}$$

$$\tau = RC \rightarrow C = .1 \mu F \rightarrow R =$$

$$f_c = 1 \rightarrow \tau = .159 \rightarrow \left| \frac{V_{out}}{V_{in}} \right| = .7$$

try

$$f_c = .1 \text{ Hz} \rightarrow \tau = 1.59 \rightarrow \left| \frac{V_{out}}{V_{in}} \right| = 1$$

$$\tau = 1.59 \quad C = 10 \mu F \quad R = 159 \text{ k}$$

This is bad

try  $f_c = 10$

$$\tau = .0159$$

$$C = .1 \mu F \Rightarrow R = 159 \text{ k}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = .999$$

## low pass

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{(1 + \tau^2 \omega^2)^{1/2}} \quad .01 = \frac{1}{(1 + \tau^2 (2\pi 4000)^2)^{1/2}} \rightarrow \tau = .0039$$

$$f_c = 100 \\ \tau = .00157 \\ R = 15.9 \text{ k} \\ C = .1 \mu F$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{(1 + \tau^2 (2\pi 850)^2)^{1/2}} = .04795$$

try double

$$\frac{V_{out}}{V_{in}} = .01 = \frac{1}{1 + \tau^2 (2\pi 4000)^2} \rightarrow \tau = .000396$$


$$\frac{1}{1 + \tau^2 (2\pi 4000)^2} = .1027$$

$$C = .1 \mu F \quad R = 3.9 \text{ k}$$

~~I~~  $1k\Omega$

$$I = \frac{V}{R}$$

Pk-Pk  
Voltage  
4.9V

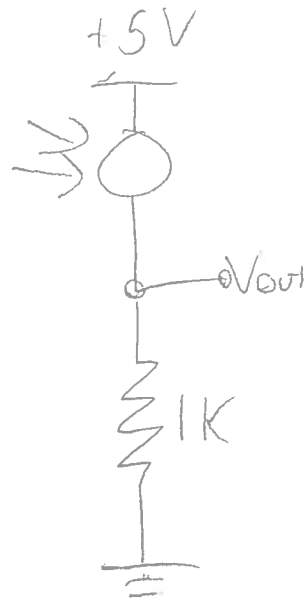

$$V_{out} = 5V \cdot \left( \frac{1k}{R_{CE} + 1k} \right)$$

High pass → want 4kHz, not 850

$$\left( \frac{V_o}{V_{in}} \right) = \frac{(\omega R)^2}{1 + \omega^2 R^2} \quad \text{for double high pass}$$


$$0.01 = \frac{(2\pi \cdot 850)^2 R^2}{1 + (2\pi \cdot 850)^2 R^2} \rightarrow R = 0.000019$$

$$\left( \frac{V_o}{V_{in}} \right) = \frac{(2\pi \cdot 4000)^2 R^2}{1 + (2\pi \cdot 4000)^2 R^2} = 0.85 \quad \text{or}$$

$$C = 1 \times 10^{-6} \text{ F} \quad R = 126 \Omega$$
  
$$R = 190 \Omega$$

amplified signal


high pass

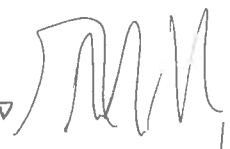

4 kHz + 850 Hz

high pass

~~low pass~~

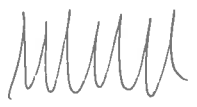

4 kHz  
~~850 Hz~~

gain 1



850 Hz

high pass subtract



$$R_3 = R_4 \quad 4x$$

~~22kΩ~~

3.3kΩ

orange / orange / red

$$2x \quad R_1 = 10k\Omega \quad \text{Brown / Black / orange}$$

$$1x \quad R_2 = 1k\Omega \quad \text{Brown / Black / red}$$




TEAM

19


Arduino = freg counter  
purpose see if signal is 850Hz or 4kHz??

Be  
right  
back



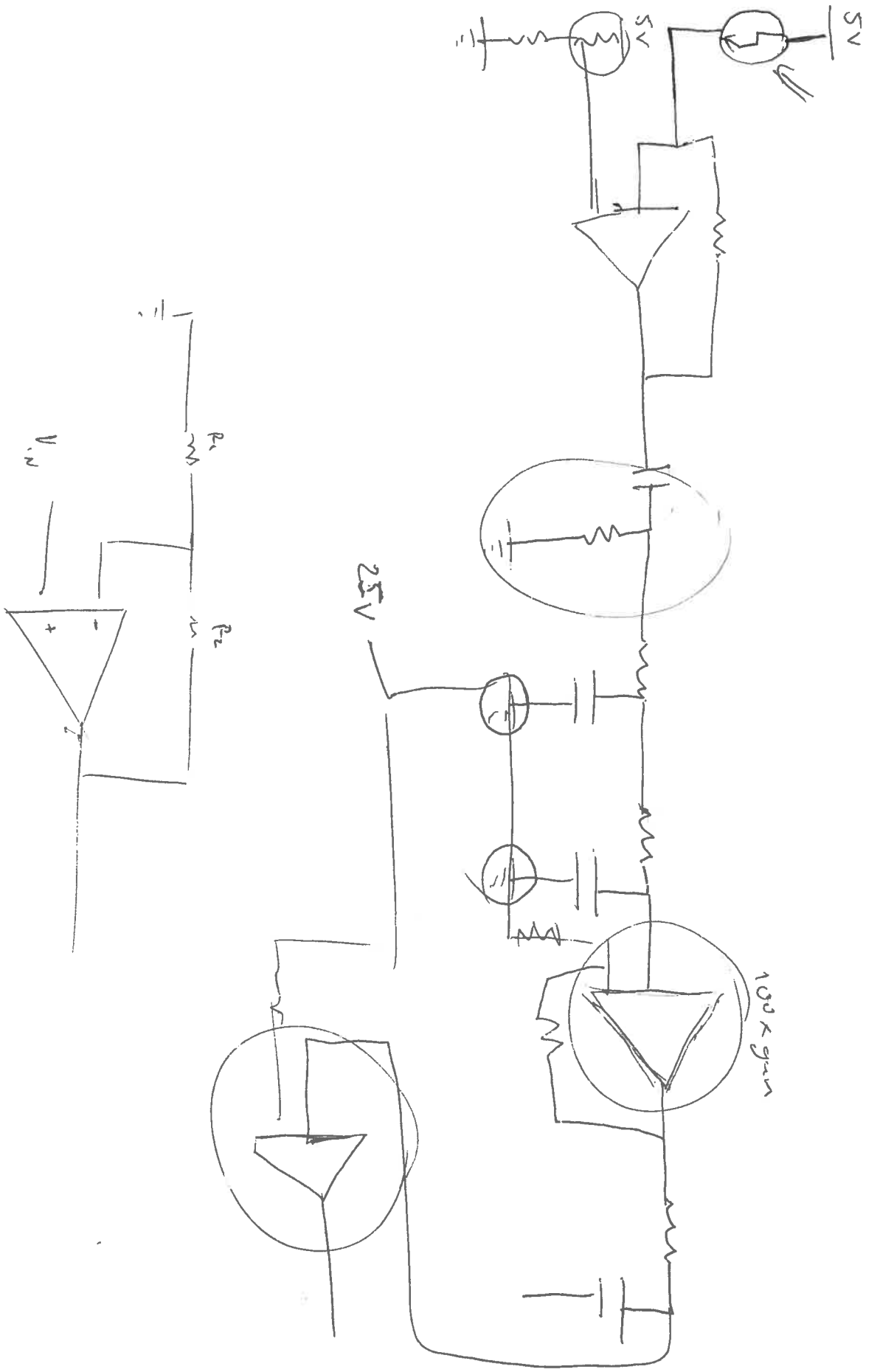

$$A_V = IR$$

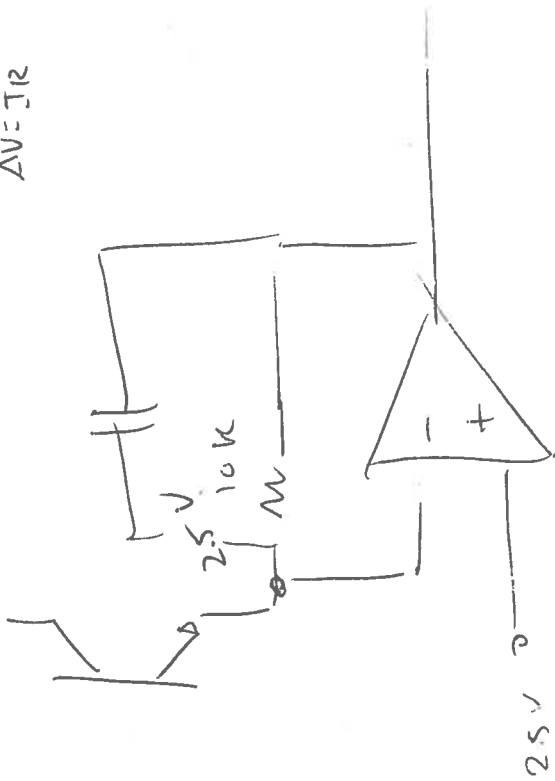

$$f_c = \frac{1}{2\pi RC} \downarrow c$$

$$\left. \begin{array}{l} 0.022 \mu F = C \\ R = 10 k \end{array} \right\}$$


$$723 \text{ Hz}$$

Low Pass

~~Low Pass~~

$$0.01 \mu F$$

$\tau_c$

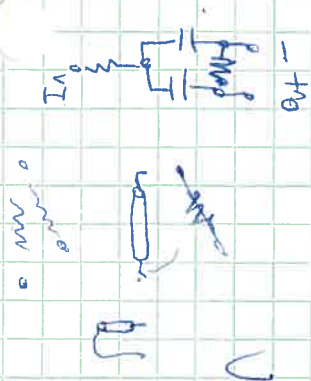

1 Pwr in  
1 GND in

8 out - Photosens  
Pwr

8 in - ~~8~~ Photosens


Signal

3 in - MUX control

~~4 out - AUX signal~~

2 out - 850/4K

E low

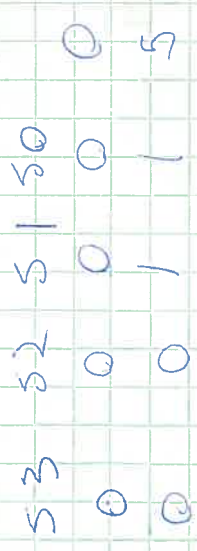

High 0-8  
Low


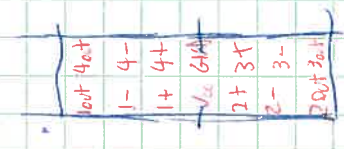
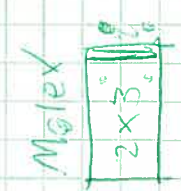
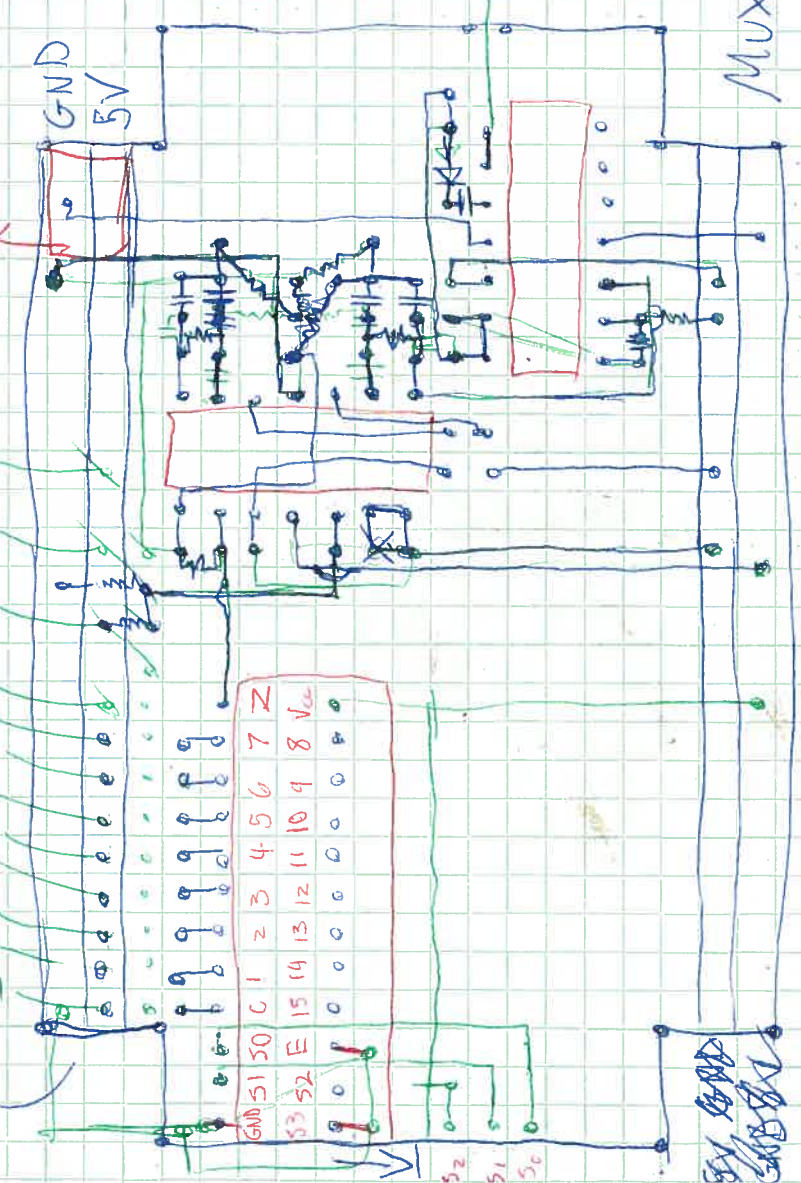
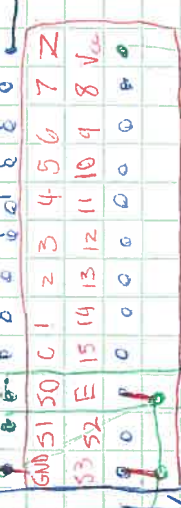



Photo sensors

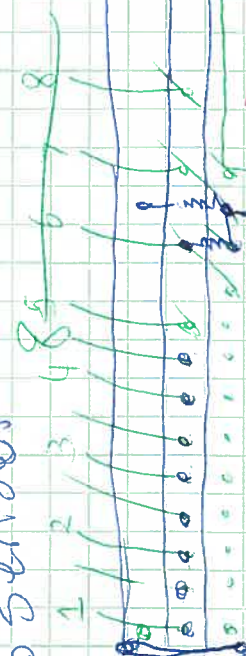

MUX - 2.5V  
- 5V

ms


1  
2  
3  
4

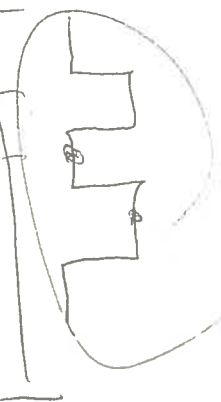

ms



0  
1

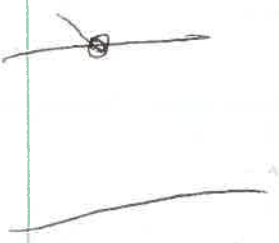

1